

ELECTRICAL CIRCUITS LABORATORY

MANUAL



DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

BALAJI INSTITUTE OF TECHNOLOGY AND SCIENCE

NARSAMPET, WARANGAL.

Vision and Mission of EEE Department

Vision:

To nurture excellence in the field of Electrical & Electronics Engineering by imparting core values to the learners and to mould the institution into a centre of academic excellence and advanced research.

Mission:

M1: To impart students with high technical knowledge to make globally adept to the new Technologies

M2: To create, disseminate and integrate knowledge of engineering, science and technology that expands the electrical engineering knowledge base towards research

M3: To provide the students with a platform for developing new products and systems that can help industry and society as a whole.

Program Outcomes

PO1	Engineering knowledge: Apply the knowledge of basic sciences and fundamental engineering concepts in solving engineering problems.
PO 2	Problem analysis: Identify and define engineering problems, conduct experiments and investigate to analyze and interpret data to arrive at substantial conclusions.
PO 3	Design/development of solutions: Propose an appropriate solution for engineering problems complying with functional constraints such as economic, environmental, societal, ethical, safety and sustainability.
PO 4	Conduct investigations of complex problems: Perform investigations, design and conduct experiments, analyze and interpret the results to provide valid conclusions.
PO 5	Modern tool usage: Select/ develop and apply appropriate techniques and IT tools for the design and analysis of the systems.
PO 6	The engineer and society: Give reasoning and assess societal, health, legal and cultural issues with competency in professional engineering practice.
PO 7	Environment and sustainability: Demonstrate professional skills and contextual reasoning to assess environmental/ societal issues for sustainable development.
PO 8	Ethics: An ability to apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
PO 9	Individual and team work: Function effectively as an individual and as a member or leader in diverse teams and in multi-disciplinary situations.
PO 10	Communication: An ability to communicate effectively.
PO 11	Project management and finance: Demonstrate apply engineering and management principles in their own / team projects in multi-disciplinary environment.
PO 12	Life-long learning: An ability to do the needs of current technological trends at electrical industry by bridging the gap between academic and industry.

Program Specific Outcomes

PSO1	Apply fundamental knowledge to identify, analyze diverse problems associated with electrical and electronic circuits, power electronics drives and power systems.
PSO2	Understand the current technological developments in Electrical & Electronics Engineering and develop the innovative products/software to cater to the needs of society & Industry.

Program Educational Objectives

PEO1	To prepare students with solid foundation in Mathematics, Sciences and Basic Engineering to cover multi-disciplinary subjects enabling them to comprehend, analyze Electrical & Electronics Engineering problems and develop solutions.
PEO2	To design and develop an electrical system component or process to meet the needs of society and industry with in realistic constraints.
PEO3	To prepare students with technical competence to use advance techniques, skills and modern engineering tools that allow them to work effectively as electrical and electronics engineer.

ATTAINMENT OF PROGRAM OUTCOMES & PROGRAM SPECIFIC OUTCOMES

Exp .No	Name of the Experiment	Program Outcomes Attained	Program Specific Outcomes Attained
1	Verification of Thevenin's and Norton's Theorems	PO1,PO2,PO3,PO9	PSO1
2	Verification of Superposition ,Reciprocity and Maximum Power Transfer theorems	PO1,PO2,PO3,PO9	PSO1
3	Locus Diagrams of RL and RC Series Circuits	PO1,PO2,PO3,PO9	PSO1
4	Series and Parallel Resonance	PO1,PO2,PO3,PO9	PSO1
5	Time response of first order RC / RL network for periodic non – sinusoidal inputs – Time constant and Steady state error determination.	PO1,PO2,PO3,PO9	PSO1
6	Two port network parameters – Z – Y parameters, Analytical verification.	PO1,PO2,PO3,PO9	PSO1
7	Two port network parameters – A, B, C, D & Hybrid parameters, Analytical	PO1,PO2,PO3,PO9	PSO1
8	Separation of Self and Mutual inductance in a Coupled Circuit. Determination of Coefficient of Coupling	PO1,PO2,PO3,PO9	PSO1
9	Verification of compensation & Milliman's theorems	PO1,PO2,PO3,PO9	PSO1
10	Harmonic Analysis of non-sinusoidal waveform signals using Harmonic Analyzer, and plotting frequency spectrum.	PO1,PO2,PO3,PO9	PSO1
11	Determination of form factor for non-sinusoidal waveform	PO1,PO2,PO3,PO9	PSO1
12	Measurement of Active Power for Star and Delta connected balanced loads	PO1,PO2,PO3,PO9	PSO1
14	Measurement of Reactive Power for Star and Delta connected balanced loads	PO1,PO2,PO3,PO9	PSO1



Prepared by

S. SRIDHAR
M.Tech(Power Electronics)
Asst. Professor
EEED

S. MALLIKARJUN REDDY
M.Tech(Power Engineering)
Head of the Department
EEED

Verified by

Head of the department

PREFACE

This Laboratory book in Electrical Measurements has been revised in order to be up to date with Curriculum changes, laboratory equipment upgrading and the latest circuit simulation.

Every effort has been made to correct all the known errors, but nobody is perfect, if you find any additional errors or anything else you think is an error, please contact the HOD/EEE at mallik95_eee@yahoo.com

The Authors thanked all the staff members from the department for their valuable Suggestion and contribution.

The author would welcome the advice and suggestions leading to the improvement of the book.

The Authors,
Department of EEE.



Safety Rules and operating Procedures	I
Laboratory Safety information	II
Guidelines for Laboratory Notebook	III
Troubleshooting Hints	IV

LABORATORY PRACTICE

SAFETY RULES

1. SAFETY is of paramount importance in the Electrical Engineering Laboratories.
2. Electricity NEVER EXECUSES careless persons. So, exercise enough care and attention in handling electrical equipment and follow safety practices in the laboratory. (Electricity is a good servant but a bad master).
3. Avoid direct contact with any voltage source and power line voltages. (Otherwise, any such contact may subject you to electrical shock)
4. Wear rubber-soled shoes. (To insulate you from earth so that even if you accidentally contact a live point, current will not flow through your body to earth and hence you will be protected from electrical shock)
5. Wear laboratory-coat and avoid loose clothing. (Loose clothing may get caught on an equipment/instrument and this may lead to an accident particularly if the equipment happens to be a rotating machine)
6. Girl students should have their hair tucked under their coat or have it in a knot.
7. Do not wear any metallic rings, bangles, bracelets, wristwatches and neck chains. (When you move your hand/body, such conducting items may create a short circuit or may touch a live point and thereby subject you to Electrical shock)
8. Be certain that your hands are dry and that you are not standing on wet floor. (Wet parts of the body reduce the contact resistance thereby increasing the severity of the shock)
9. Ensure that the power is OFF before you start connecting up the circuit. (Otherwise you will be touching the live parts in the circuit).
10. Get your circuit diagram approved by the staff member and connect up the circuit strictly as per the approved circuit diagram.
11. Check power chords for any sign of damage and be certain that the chords use safety plugs and do not defeat the safety feature of these plugs by using ungrounded plugs.
12. When using connection leads, check for any insulation damage in the leads and avoid such defective leads.
13. Do not defeat any safety devices such as fuse or circuit breaker by shorting across it. Safety devices protect YOU and your equipment.
14. Switch on the power to your circuit and equipment only after getting them checked up and approved by the staff member.

15. Take the measurement with one hand in your pocket. (To avoid shock in case you accidentally touch two points at different potentials with your two hands)
16. Do not make any change in the connection without the approval of the staff member.
17. In case you notice any abnormal condition in your circuit (like insulation heating up, resistor heating up etc), switch off the power to your circuit immediately and inform the staff member.
18. Keep hot soldering iron in the holder when not in use.
19. After completing the experiment show your readings to the staff member and switch off the power to your circuit after getting approval from the staff member.
20. Determine the correct rating of the fuse/s to be connected in the circuit after understanding correctly the type of the experiment to be performed: no-load test or full-load test, the maximum current expected in the circuit and accordingly use that fuse-rating.(While an over-rated fuse will damage the equipment and other instruments like ammeters and watt-meters in case of over load, an under-rated fuse may not allow one even to start the experiment)
21. Moving iron ammeters and current coils of wattmeters are not so delicate and hence these can stand short time overload due to high starting current. Moving iron meters are cheaper and more rugged compared to moving coil meters. Moving iron meters can be used for both a.c. and d.c. measurement. Moving coil instruments are however more sensitive and more accurate as compared to their moving iron counterparts and these can be used for d.c. measurements only. Good features of moving coil instruments are not of much consequence for you as other sources of errors in the experiments are many times more than those caused by these meters.
22. Some students have been found to damage meters by mishandling in the following ways:
 - i. Keeping unnecessary material like books, labrecords, unused meters etc. causing meters to fall down the table.
 - ii. Putting pressure on the meter (especially glass) while making connections or while talking or listening somebody.

STUDENTS ARE STRICTLY WARNED THAT FULL COST OF THE METER WILL BE RECOVERED FROM THE INDIVIDUAL WHO HAS DAMAGED IT IN SUCH A MANNER.

Copy these rules in your Lab Record. Observe these yourself and help your friends to observe.



I have read and understand these rules and procedures. I agree to abide by these rules and procedures at all times while using these facilities. I understand that failure to follow these rules and procedures will result in my immediate dismissal from the laboratory and additional disciplinary action may be taken.

Signature

Date

Lab



GUIDELINES FOR LABORATORY NOTEBOOK

The laboratory notebook is a record of all work pertaining to the experiment. This record should be sufficiently complete so that you or anyone else of similar technical background can duplicate the experiment and data by simply following your laboratory notebook. Record everything directly into the notebook during the experiment. Do not use scratch paper for recording data. Do not trust your memory to fill in the details at a later time.

Organization in your notebook is important. Descriptive headings should be used to separate and identify the various parts of the experiment. Record data in chronological order. A neat, organized and complete record of an experiment is just as important as the experimental work.

1. Heading:

The experiment identification (number) should be at the top of each page. Your name and date should be at the top of the first page of each day's experimental work.

2. Object:

A brief but complete statement of what you intend to find out or verify in the experiment should be at the beginning of each experiment

3. Diagram:

A circuit diagram should be drawn and labeled so that the actual experiment circuitry could be easily duplicated at any time in the future. Be especially careful to record all circuit changes made during the experiment.

4. Equipment List:

List those items of equipment which have a direct effect on the accuracy of the data. It may be necessary later to locate specific items of equipment for rechecks if discrepancies develop in the results.

5. Procedure:

In general, lengthy explanations of procedures are unnecessary. Be brief. Short commentaries alongside the corresponding data may be used. Keep in mind the fact that the experiment must be reproducible from the information given in your notebook.

6. Data:

Think carefully about what data is required and prepare suitable data tables. Record instrument readings directly. Do not use calculated results in place of direct data; however, calculated results may be recorded in the same table with the direct data. Data tables should be clearly identified and each data column labeled and headed by the proper units of measure.

7. Calculations:

Not always necessary but equations and sample calculations are often given to illustrate the treatment of the experimental data in obtaining the results.

8. Graphs:

Graphs are used to present large amounts of data in a concise visual form. Data to be presented in graphical form should be plotted in the laboratory so that any questionable data points can be checked while the experiment is still set up. The grid lines in the notebook can be used for most graphs. If special graph paper is required, affix the graph permanently into the notebook. Give all graphs a short descriptive title. Label and scale the axes. Use units of measure. Label each curve if more than one on a graph.



9. Results:

The results should be presented in a form which makes the interpretation easy. Large amounts of numerical results are generally presented in graphical form. Tables are generally used for small amounts of results. Theoretical and experimental results should be on the same graph or arranged in the same table in a way for easy correlation of these results.

10. Conclusion:

This is your interpretation of the results of the experiment as an engineer. Be brief and specific. Give reasons for important discrepancies.

TROUBLE SHOOTING HINTS

1. Be Sure that the power is turned ON
2. Be sure the ground connections are common
3. Be sure the circuit you build is identical to your circuit diagram (Do a node by node check)
4. Be sure that the supply voltages are correct
5. Be sure that the equipment is set up correctly and you are measuring the correct parameters
6. If steps 1 through 5 are correct then you probably have used a component with the wrong value or one that doesn't work. It is also possible that the equipment does not work (although this is not probable) or the protoboard you are using may have some unwanted paths between nodes. To find your problem you must trace through the voltages in your circuit node by node and compare the signal you expect to have. Then if they are different use your engineering judgment to decide what is causing the different or ask your lab assistant.

ELECTRICAL CIRCUITS LABORATORY



LIST OF EXPERIMENTS

1	Verification of Thevenin's and Norton's Theorems
2	Verification of Superposition, Reciprocity and Maximum Power Transfer theorems
3	Locus Diagrams of RL and RC Series Circuits
4	Series and Parallel Resonance
5	Time response of first order RC / RL network for periodic non – sinusoidal inputs – Time constant and Steady state error determination.
6	Two port network parameters – Z – Y parameters, Analytical verification.
7	Two port network parameters – A, B, C, D & Hybrid parameters, Analytical
8	Separation of Self and Mutual inductance in a Coupled Circuit. Determination of Coefficient of Coupling
9	Verification of compensation & Milliman's theorems
10	Harmonic Analysis of non-sinusoidal waveform signals using Harmonic Analyzer, and plotting frequency spectrum.
11	Determination of form factor for non-sinusoidal waveform
12	Measurement of Active Power for Star and Delta connected balanced loads
14	Measurement of Reactive Power for Star and Delta connected balanced loads

THEVENIN'S THEOREM


Aim: To verify and prove the Thevenin's Theorem

Apparatus Required:

Sl.no	Name of the equipment	Range/Type	Quantity
1	Dual Regulated power supply	(0-30V)/2A DC	1 no.
2	Digital multimeter Modes DC ammeter DC volt meter Ohmmeter	(0-200mA) (0-20V) (0- 2kΩ)	1 no.
3	Resistors	R ₁ =120 R ₂ =330 R ₃ =560 R ₄ =680 R ₅ =820	1 No. each
4	Bread board	-----	1No.
5	Connecting Wires	-----	Required

Theory:

Thevenin's Theorem: It is defined as that in any two terminal linear bilateral network which contains one or more sources can be replaced by a single voltage source with a series resistor.

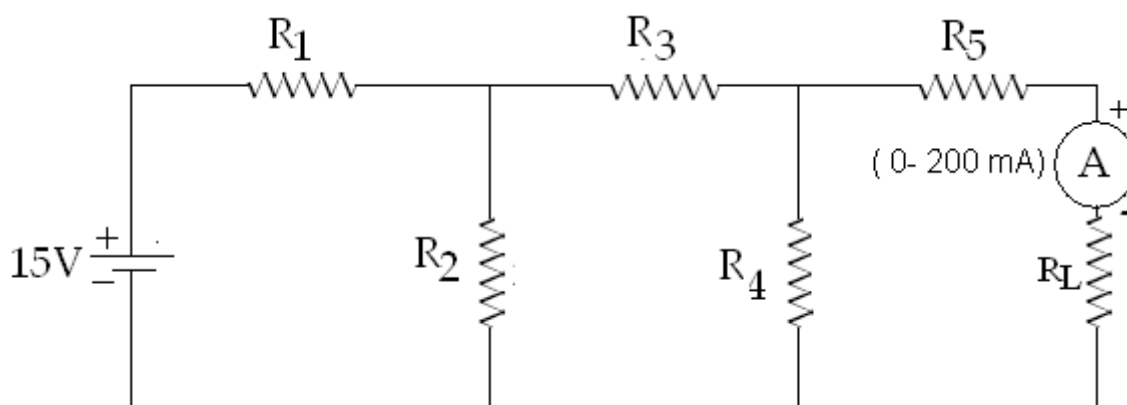Circuit Diagrams:

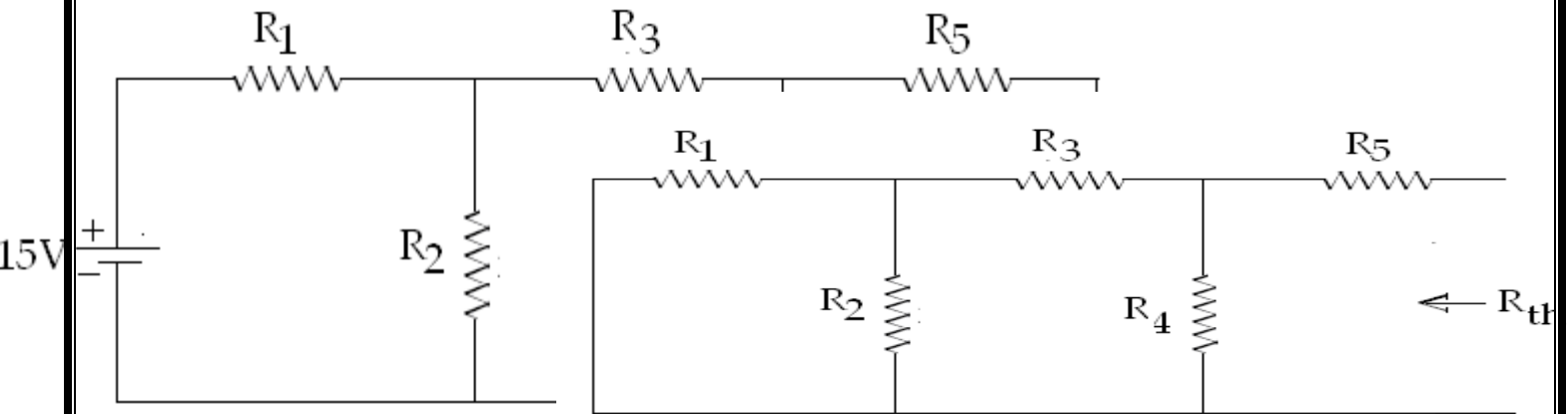


Fig.1

V_{th}

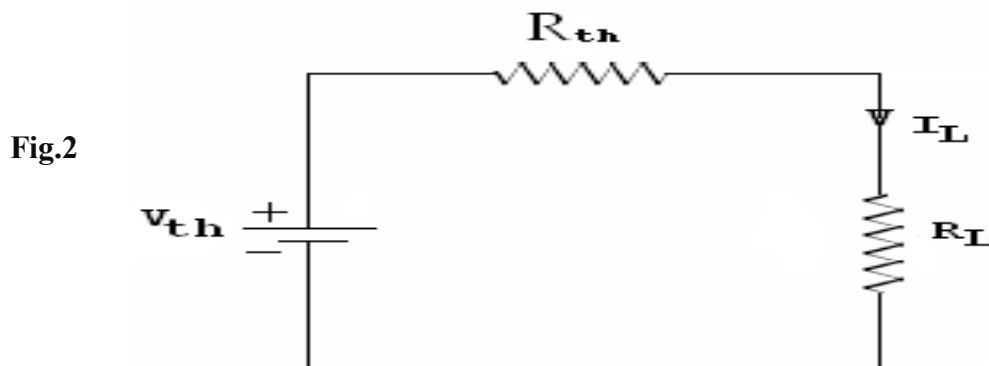


Fig.2

Procedure:

1. Connect the circuit as per the circuit diagram shown in fig(1).
2. By applying the input voltage and connecting the load resistance at the output terminals measure the load current I_{L1} as shown in fig (1).
3. Connect the circuit diagram shown in fig (2) measure the thevenin's voltage V_{th} .
4. Connect the circuit diagram shown in fig (3) and Measure the thevenin's resistance using digital multimeter.
5. Connect the thevenin's equivalent circuit and measure the load current I_{L2} . ($I_{L1} = I_{L2}$)

Tabular Form:


	Source Voltage (Vs)	Thevenin's voltage V_{th} .	Thevenin's Resistance R_{th}	Current(I_{L1}) mA (fig-1)	Current(I_{L2}) mA (fig-4)
Theoretical values					
Practical values					

Result: Hence the Thevenin's theorem is verified theoretically and practically.


THEVENINS THEOREM

Practice problems:


Question 1: Using Thevenin's theorem, find the current through branch AB for the below circuit?

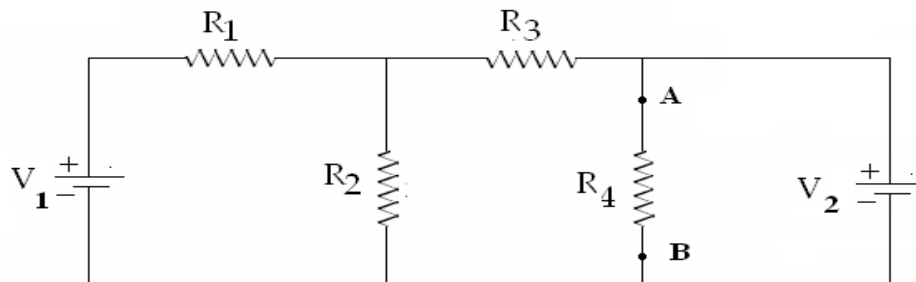

Question 2: Using Thevenin's theorem, find the current through branch AB in which a galvanometer is connected for the below circuit?

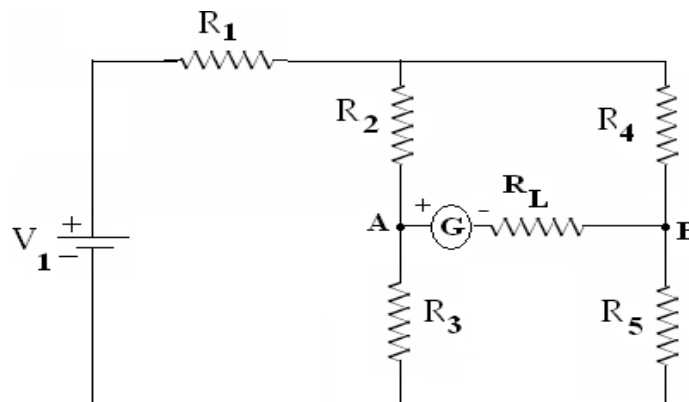

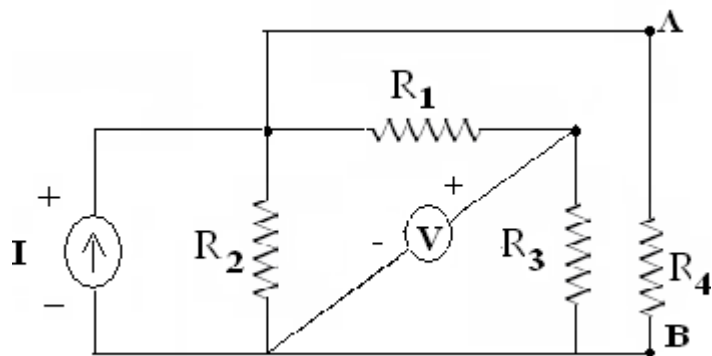Question 3: Using Thevenin's theorem, find the current through branch AB in the below circuit?



NORTON'S THEOREM

Aim: To Verify Norton's theorem.

Apparatus Required:

Sl.no	Name of the equipment	Range/Type	Quantity
1	Dual Regulated power supply	(0-30V)/2A	1 no.
2	Digital multimeter		1 no.

	Modes	DC ammeter DC volt meter Ohmmeter	(0-200mA) (0-20V) (0- 2k Ω)	
3	Resistors		R ₁ = 120 R ₂ = 330 R ₃ = 560 R ₄ = 680 R ₅ = 820	1No. each
4	Connecting Wires		-----	Required
5	Breadboard		-----	1No

Norton's Theorem:

It is defined as that in any two terminal linear bilateral network which contains one or more sources can be replaced by a single current source with a parallel resistor.

Circuit Diagram:

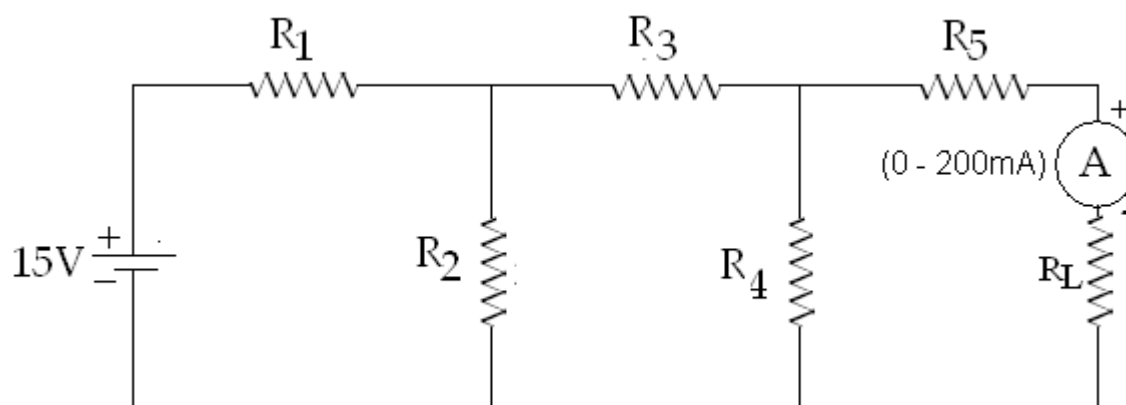


Fig.1

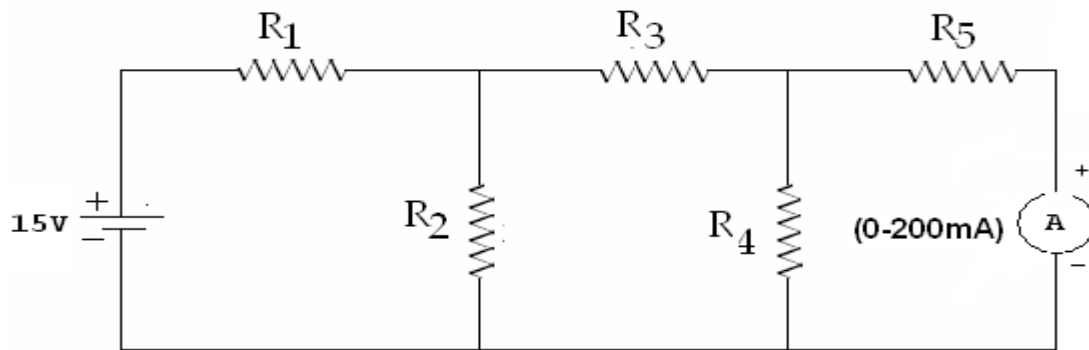


Fig. 2

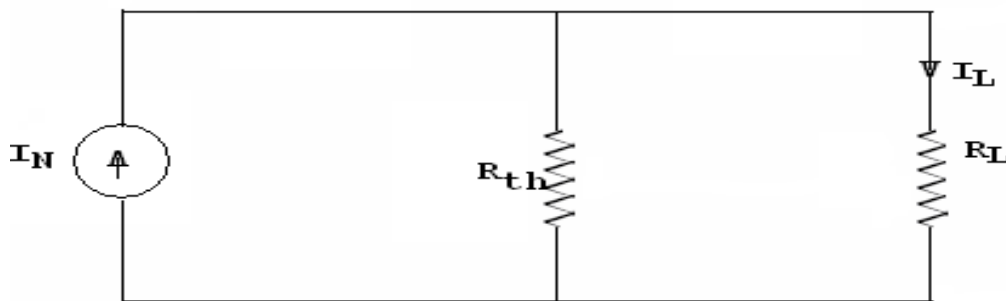


Fig.3

Procedure:

1. Connect the circuit diagram as shown in fig.1 and measure the load current I_{L1} .
2. Connect the circuit diagram as shown in fig.2 and measure the Norton's equivalent current I_N .
3. Connect the Norton's equivalent circuit and determine the load current I_{L2} .
4. Verify $I_{L1} = I_{L2}$.

Tabular Form:

	Source Voltage (Vs)	Norton's current I_N (mA).	Current(I_{L1}) mA	Current(I_{L2}) mA
Theoretical values				
Practical values				


Result:

Hence Norton's theorem is verified theoretically and practically.


NORTON'S THEOREM

Practice Problems:


Question 1: Using Norton's theorem, find the current through branch AB for the below circuit?

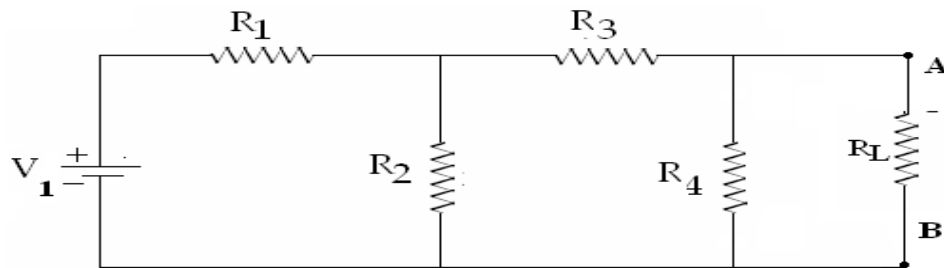

Question 2: Find V_o in the circuit using Norton's Theorem?

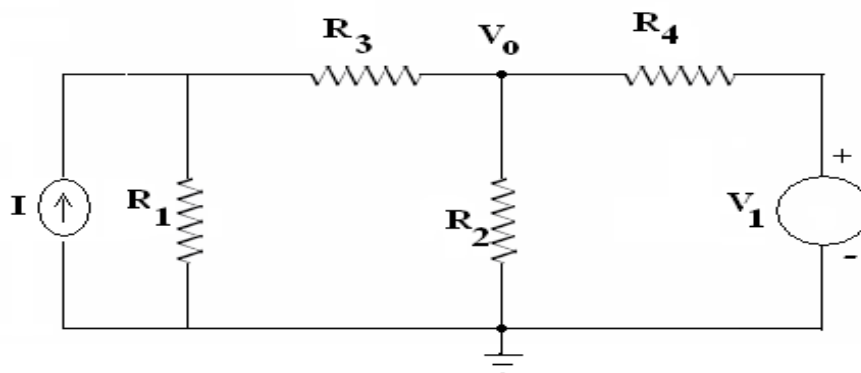

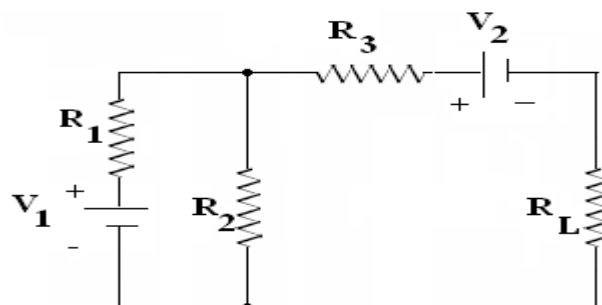Question 3: Find the current through R_L resistor, using Norton's Theorem?



RECIPROCITY THEOREM

Aim: To verify reciprocity theorem.

Apparatus required:

<i>Sl. No</i>	<i>Name of equipment</i>	<i>range</i>	<i>quantity</i>
1	Dual Regulated power supply	(0–30 V)/ 2A	1 no
2	Digital Multimeter		1 no
	Voltmeter mode	0-20V	
	Ammeter mode	0-200 mA	
3	Resistors		
	R1	510ohm	1 no. each
	R2	1kohm	
	R3	220ohm	

4	Bread Board	-----	1 no.
5	Connecting wires	-----	Required


Statement of Reciprocity Theorem:

In any branch of a network, the current due to a single source of voltage(V) elsewhere in the network is equal to the current through the branch in which the source was originally placed when the source is placed in the branch in which the current (I) was originally obtained.

Theory:

In a linear, bilateral, single source network if a voltage at any point in the network produces a current at some other point in the network, then the same voltage at the other point produces the same current at the first point.

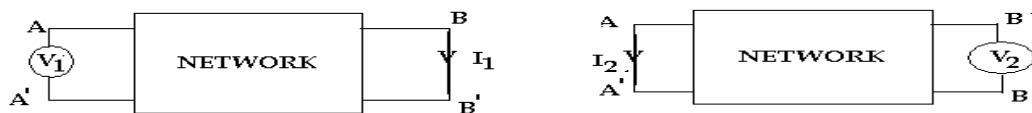The ratio of response to excitation is same. Reciprocity theorem is applicable for single voltage and single current source networks only.



Voltage V_1 across AA^1 produces current I_1 at BB^1 . Now if the positions of the source and responses are interchanged, by connecting the voltage source across BB^1 , the resultant current I_2 will

be at terminals AA¹. According to reciprocity theorem, the ratio of response to excitation is same in both the cases.

$$\text{i.e. } I_1 / V_1 = I_2 / V_2$$

The location of the voltage source and the through current may be interchanged with out change in current. However, the polarity of the voltage source should have the identity with the direction of branch current in each position.

According to this theorem if the source voltage and zero resistance ammeter are changed, the magnitude of the current through the ammeter will be same, no matter how completed the network. In other words, in a linear passive network, supply voltage V & current I are mutually transferable. The ratio of V and I is called the transfer resistance.

The limitation of this theorem is that it is only applicable to single source networks and not in multisource network. More over the network should not have any time varying element.

Circuit diagram

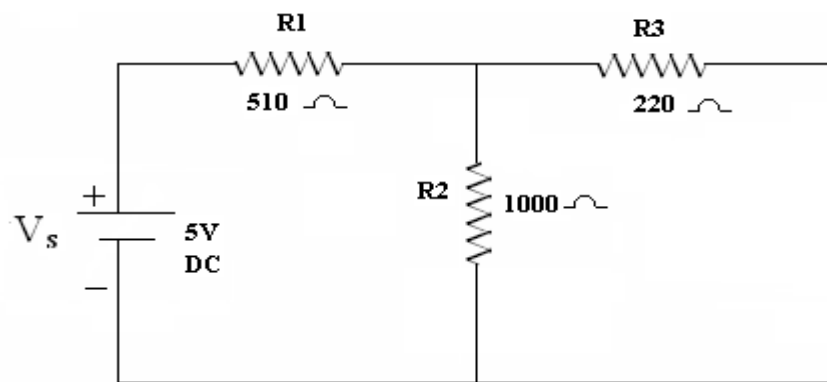


Fig (i)

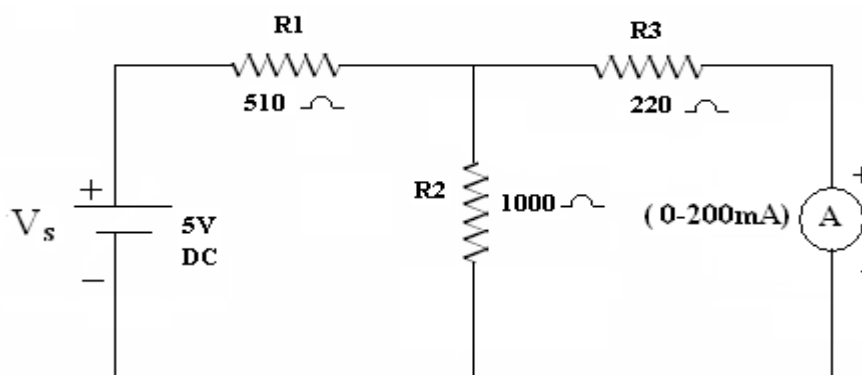


Fig (ii)

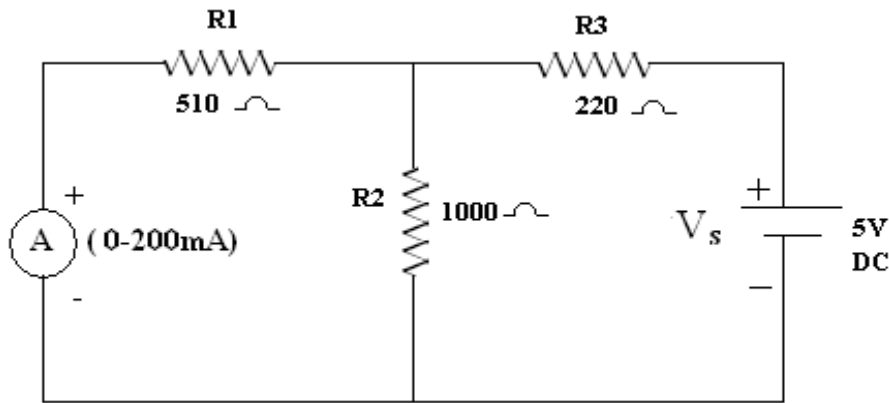


Fig (iii)

Procedure:

The experiment of verification of reciprocity theorem can be performed in the following steps.

1. Connect the circuit as per the circuit diagram.
2. note down the reading of current using an ammeter in 220 ohm resistor branch as shown in fig (i)
3. Now interchange the source and ammeter and note down the current reading in 120ohm resistor branch as shown in fig(ii)
4. Calculate the currents theoretically for the currents shown in fig (i) & fig (ii).
5. Enter the theoretical and practical values in a tabular column.

Tabular column:

	V _s (volts)	I ₁ (mA)	I ₂ (mA)	I ₁ /V _s	I ₂ /V _s
Theoretical					
Practical					

Result: It is observed that the values of currents I₁ & I₂ obtained are approximately equal with in limits of experimental errors, thus the reciprocity theorem stands verified.

SUPERPOSITION THEORM

Aim :- To verify the superposition theorem.


Apparatus required :-

Sl.no.	Name of equipment	range	quantity
1	Dual Regulated power supply	(0-30 V)/2A	1 no
2	Digital Multimeter Voltmeter mode Ammeter mode	0-20V 0-200mA	1 no
3	Resistors R1 R2 R3	510 Ω 1k Ω 220 Ω	1 no. each
4	Bread board	----	1 no
5	Connecting wires	-----	Required


Statement of Superposition Theorem :

In a network of linear resistances containing more than one source of e.m.f, the current which flows at any point is the sum of all the currents which would flow at that point if each source of e.m.f were considered separately and all the other sources of e.m.f's replaced for the time being by resistances equal to their internal resistances.

CIRCUIT DIAGRAM:-

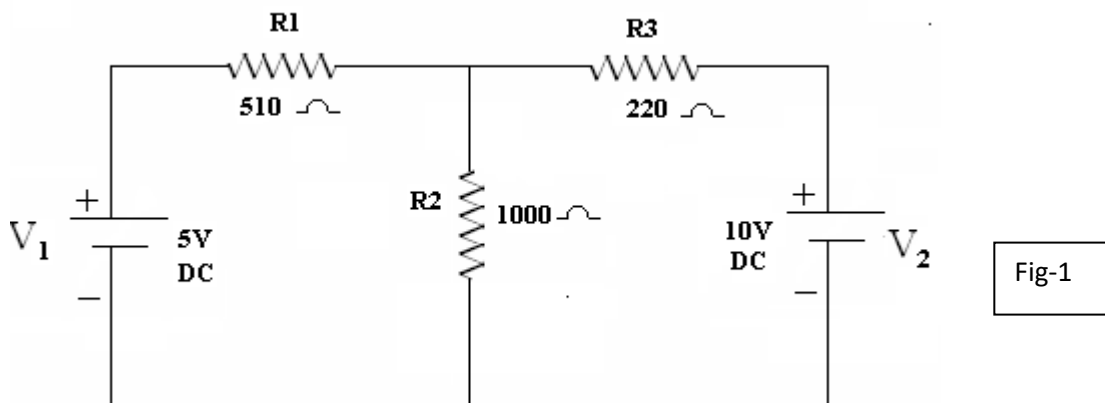

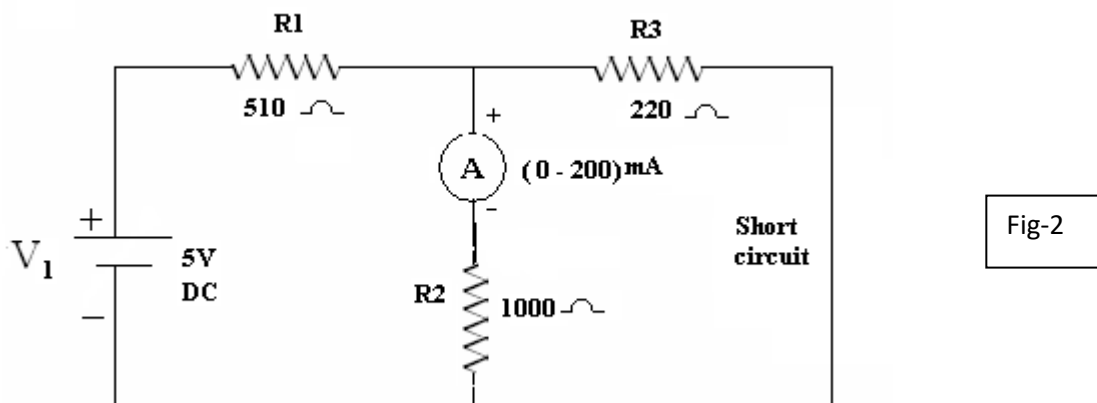- i) Circuit to find current in 1K ohm resistor due to 5V source (short the terminals of 10V source) for fig-2.



- ii) Circuit to find current in 1000ohm resistor due to 10V source (short the terminals of 5V source) for fig-3

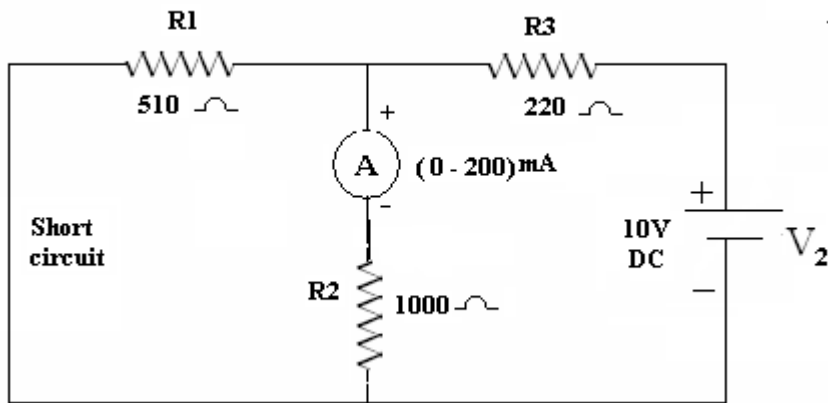


Fig-3

- iii) Circuit to find current in 1000ohm resistor due to 10V source & 5V source acting simultaneously for fig-4.

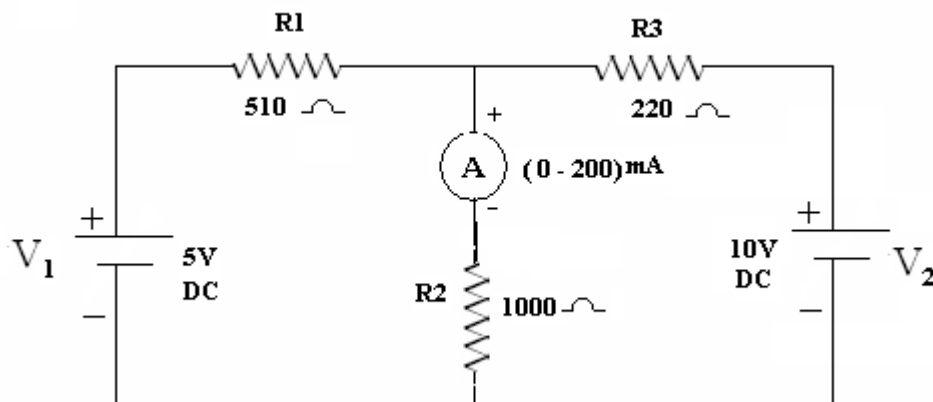


Fig-4

Procedure :-

1. Make the connections as per circuit diagram.
2. Short circuit the 10V source and take the reading of current in 1000ohm resistor using an ammeter due to 5V source (as seen in fig(i))
3. Now shortcircuit the 5V source and note down the reading of current in 1000ohm resistor using an ammeter due to 10V source(as seen in fig(ii))
4. Note down the reading of current using an ammeter in 1000ohm resistor due to 10V source and 5V source acting simultaneously.
5. Theoretical calculations of currents due to individual sources and both sources acting simultaneously are to be taken.
6. Compare theoretical (I_1 , I_2 , & I) and practical values and these are to be tabulated.

Observation table :-

	I_1 (mA)	I_2 (mA)	$I = I_1 + I_2$ (mA)

Theoretical			
Practical			

RESULT: - It is observed that the values of currents I_1 & I_2 obtained are approximately equal with in limits of experimental errors, thus the superposition theorem stands verified.

MAXIMUM POWER TRANSFER THEOREM

Aim: To Verify the maximum power transfer theorem.


Apparatus Required:

Sl.no	Name of the equipment	Range/Type	Quantity
1	Dual Regulated power supply	(0-30V)/2A DC	1 no.
2	Digital multimeter Modes DC ammeter DC volt meter Ohmmeter	(0-200mA) (0-20V) (0- 2k Ω)	1 no.
3	Resistors	$R_1 = 100 \Omega$ $R_2 = 100 \Omega$ $R_3 = 560 \Omega$	1 no. each
4	Decay Resistance Box	-----	1 no.
5	Connecting Wires	-----	Required

Statement of Max. Power Transfer Theorem:

A resistive load will abstract maximum power from a network when the load resistance is equal to the resistance of the network as viewed from the output terminals, with all the energy sources removed leaving behind their internal resistance.

Circuit Diagram:

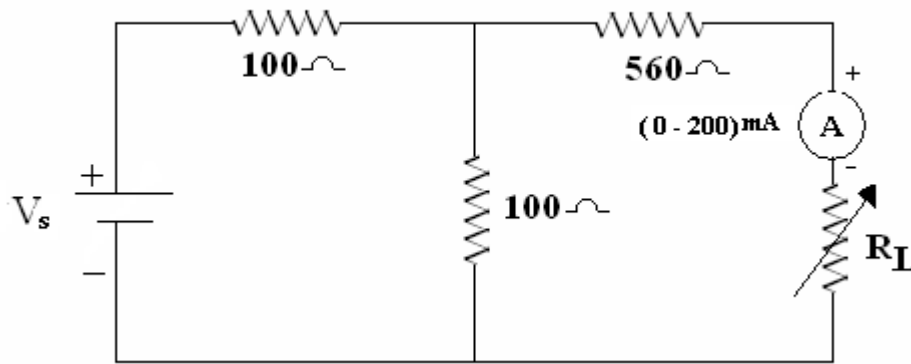**Procedure:**


1. Connections are made as per the circuit diagram.
2. At some constant voltage, by varying the load resistance note down the readings of voltmeter and ammeter.
3. Calculate the power delivered to the load.
4. Find out the internal resistance at which maximum power is transmitted to the load.
5. Calculate the internal resistance of the circuit theoretically and verify with the resistance where we got the maximum power.
6. Draw the graph between powers delivered to load Vs load resistance.

Tabular Form:

S.no	$R_L \Omega$	$I_L(\text{mA})$ (Theoretical)	$P=I^2R_L(\text{mW})$ (Theoretical)	$I_L(\text{mA})$ (Practical)	$P=I^2R_L(\text{mW})$ (Practical)

Model Graph:

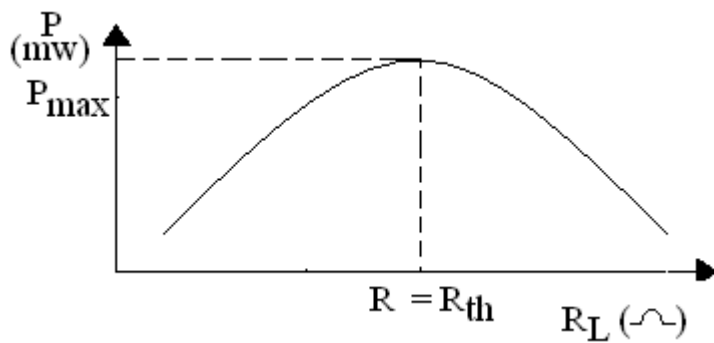A graph is plotted between load resistance R_L and power P . Taking R_L on X-axis and power on Y-axis. At the particular resistance value i.e. R_{th} the power will be maximum.



Calculations:

- By open circuiting the load terminals calculate the Thevenin's voltage V_{th} across the load terminals.
- By replacing all voltage and current sources with their internal resistances, calculate the Thevenin's resistance R_{th} across the load terminals.
- Draw the Thevenin's equivalent circuit, calculate the load current $I_L = V_{th} / (R_{th} + R_L)$.
- The power delivered to the load $= I_L^2 R_L$.
- The power is maximum at R_{th} .

Result:

Maximum power transfer theorem is verified theoretically and practically

TWO PORT NETWORK PARAMETERS

Aim: To Determine Z and Y parameters of a given two port network.

Apparatus required:

Sl.no	Name of the equipment	Range/Type	Quantity
1	Dual Regulated power supply	(0-30V)/2A	1 no.
2	Digital multimeter Modes DC ammeter DC volt meter Ohmmeter	(0-200mA) (0-20V) (0- 2k Ω)	1 no.

3	Resistors	$R_1 = 100 \Omega$ $R_2 = 100 \Omega$ $R_3 = 560 \Omega$	
4	Decay Resistance Box(option)	-----	1 no.
5	Connecting Wires	-----	Req.

Z Parameters:

Theory: Z Parameters are also known as open circuit or impedance parameters. In Z parameters V_1 and V_2 are dependent variables and I_1 and I_2 are independent variables.

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Where Z_{11} , Z_{12} , Z_{21} , Z_{22} are the network functions and are known as impedance parameters.

$Z_{11} = V_1 / I_1$ when $I_2=0$ is called driving point impedance.

$Z_{21} = V_2 / I_1$ when $I_2=0$ is called forward transfer impedance.

$Z_{12} = V_1 / I_2$ when $I_1=0$ is called reverse transfer impedance.

$Z_{22} = V_2 / I_2$ when $I_1=0$ is called driving point impedance.

Determination of Z_{11} and Z_{21} when $I_2 = 0$

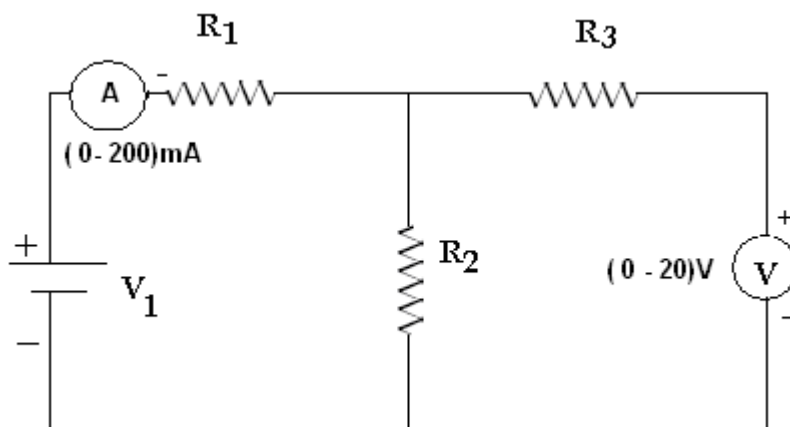


Fig.1

Tabular Form:

Parameter	V_1	I_1	V_2
Theoretical			
Practical			

Determination of Z_{12} and Z_{22} when $I_1 = 0$

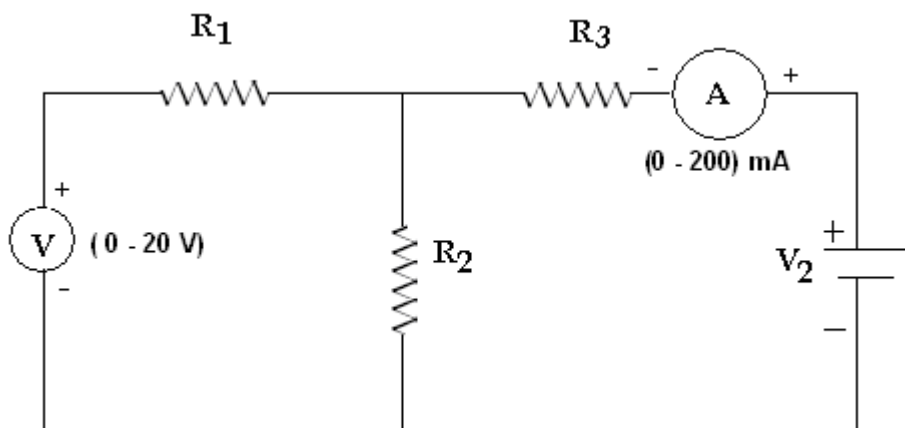


Fig.2

Tabular Form:

Parameter	V_2	V_1	I_2
Theoretical			
Practical			

Procedure:

1. For measuring Z_{11} and Z_{21} make the connections as shown in Fig(1).
2. Connect port 1 to RPS, apply 10V at port 1 and measure I_1 and V_2 .
3. For measuring Z_{12} and Z_{22} make the connections as shown in Fig (2).
4. Connect RPS to port 2, apply 10 V at port 2 and measure I_2 , V_2 .

5. Determine the Z Parameters.

Z – Parameters:

Parameter	$Z_{11} = V_1 / I_1$	$Z_{12} = V_1 / I_2$	$Z_{21} = V_2 / I_1$	$Z_{22} = V_2 / I_2$
Theoretical				
Practical				

Y PARAMETERS:

Theory:

Y Parameters are also known as short circuit or admittance parameters. In Y Parameters I_1 and I_2 are dependent variable and V_1 , V_2 are independent variables.

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Here Y_{11} , Y_{12} , Y_{21} , Y_{22} are the network functions called as admittance parameters.

$$Y_{11} = I_1 / V_1 \quad \text{when } V_2 = 0$$

$$Y_{21} = I_2 / V_1 \quad \text{when } V_2 = 0$$

$$Y_{12} = I_1 / V_2 \quad \text{when } V_1 = 0$$

$$Y_{22} = I_2 / V_2 \quad \text{when } V_1 = 0$$

Determination of Y_{11} and Y_{21} when $V_2=0$

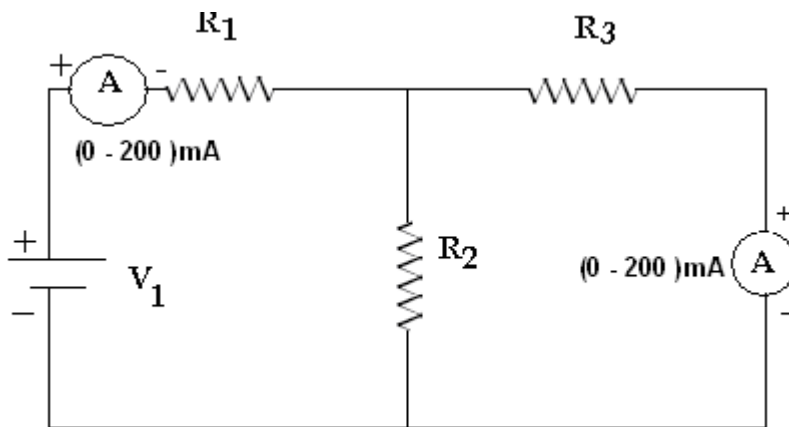


Fig.3

Tabular Form:

Parameter	V_1	I_1	I_2
Theoretical			
Practical			

Determination of Y_{12} and Y_{22} when $V_1=0$

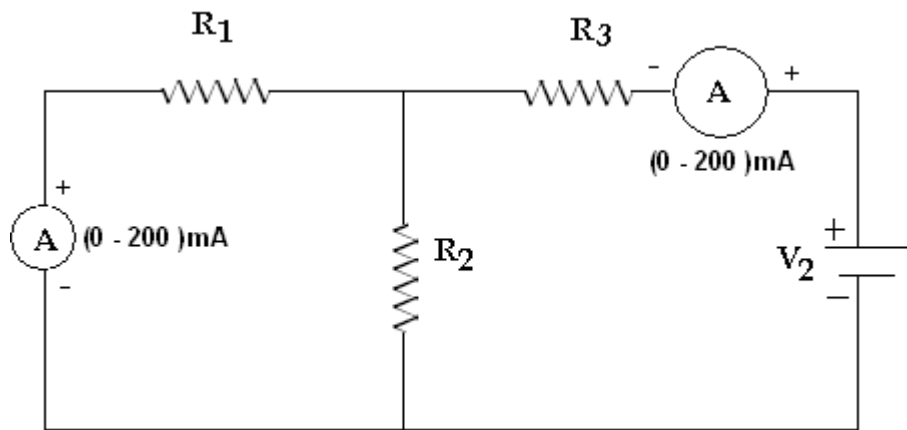


Fig.4

Tabular Form:

Parameter	I_1	I_2	V_2
Theoretical			
Practical			

Procedure:

1. For measuring Y_{11} , Y_{21} make the connections as shown in Fig (3).
2. Connect port 1 to RPS; apply 10 V at port 1 and short circuit the port 2 through an ammeter. Note down V_1 , I_1 and I_2 values.
3. For measuring Y_{12} , Y_{22} make the connections as shown in Fig (4).
4. Connect port 2 to RPS, apply 10 V at port 2 and short circuit the port 1 through an ammeter. Note down V_2 , I_2 , I_1 values.
5. Calculate the Y Parameters.

Y Parameters:


Parameter	$Y_{11} = I_1 / V_1$	$Y_{12} = I_1 / V_2$	$Y_{21} = I_2 / V_1$	$Y_{22} = I_2 / V_2$
Theoretical				
Practical				

Result: It is observed that the values of parameters obtained are approximately equal with in limits of experimental errors, thus the Y & Z parameters stands verified.


MAXIMUM POWER TRANSFER THEOREM

Practice Problems:

Question 1: Find the Value of R_L for the maximum power to transfer from source to load?

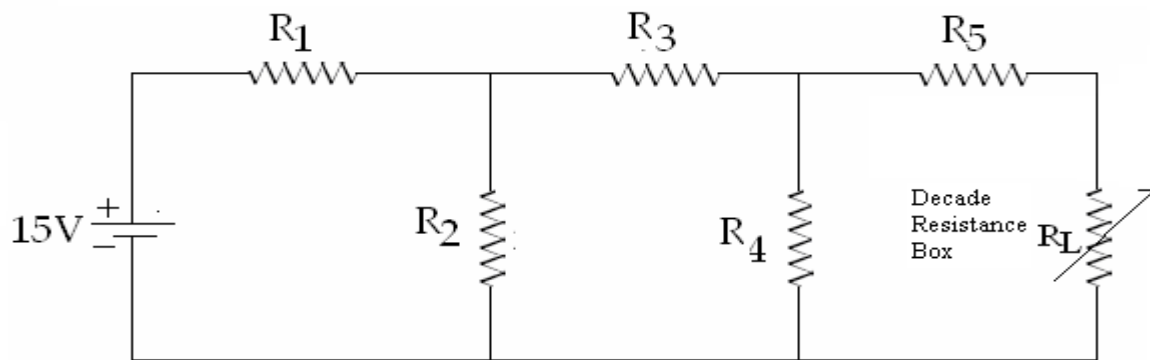

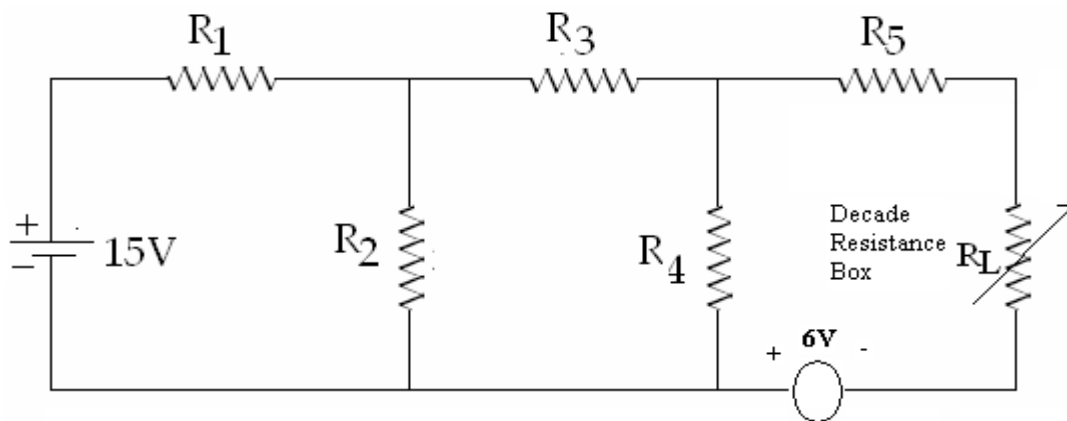
Question 2: Find the Value of R in the circuit such that Max. Power transfer takes place. What is the amount of this power?




SUPERPOSITION THEOREM

Practice Problems:

Question 1: Find the current through the R_3 Resistor using Superposition theorem?

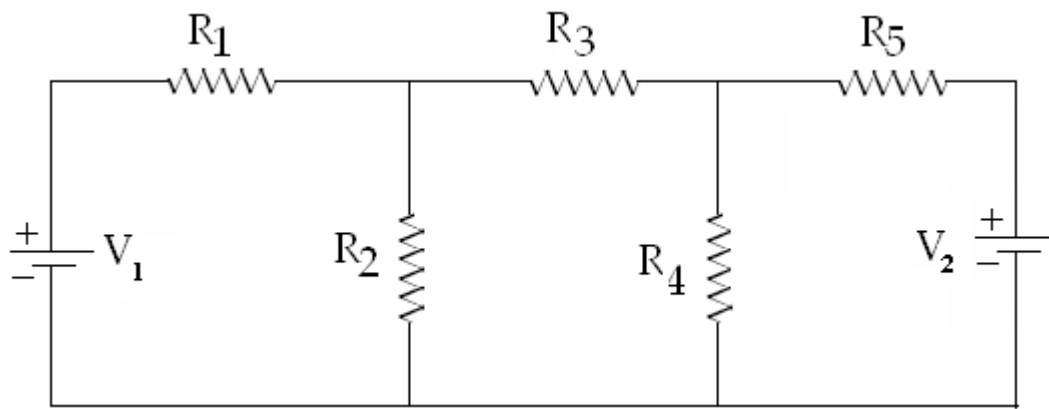

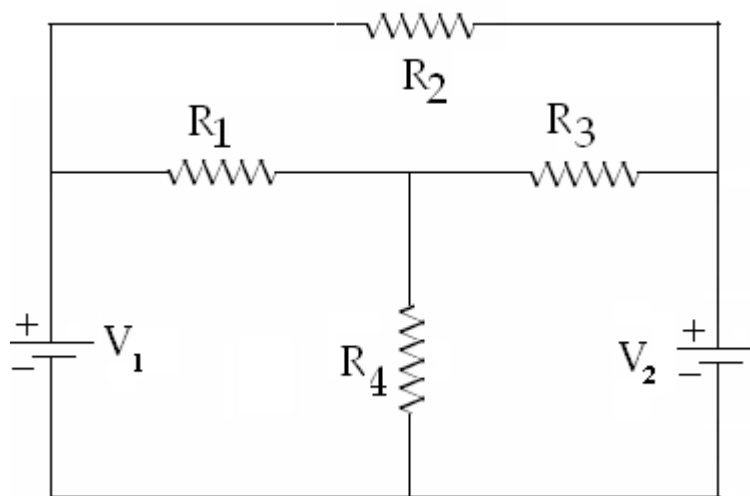
Question 2: Using Superposition, find current in R_4 Resister?




RECIPROCITY THEOREM

Practice Problems:

Question 1: Verify the Reciprocity theorem at the branch AB for the below circuit?

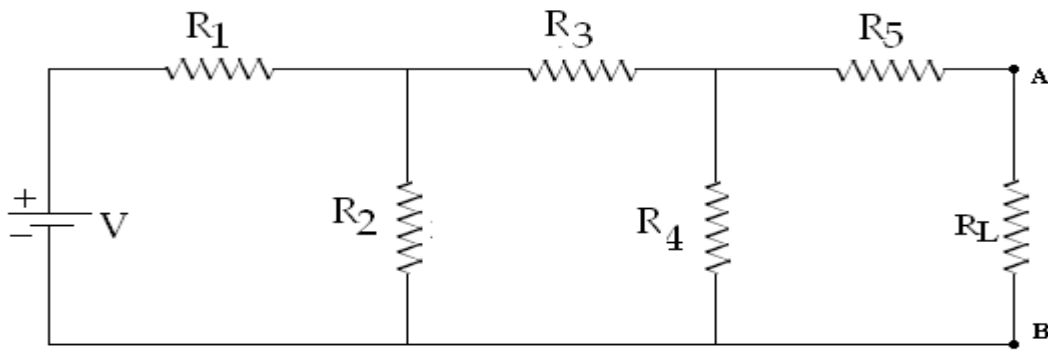

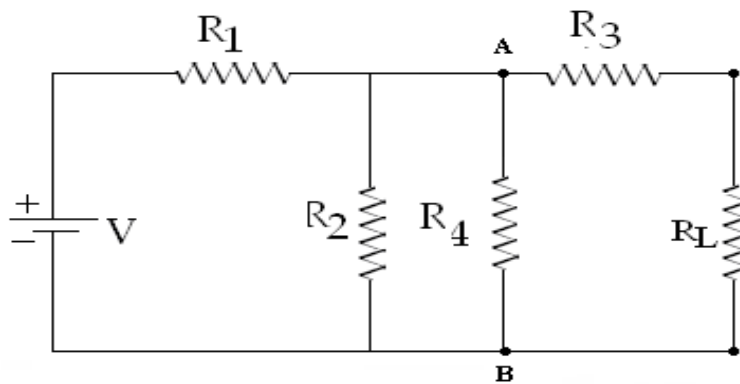
Question 2: Verify reciprocity theorem, at the terminals AB for a network when excited by a single source?




MILLMANN'S THEOREM

Practice Problems:

Question 1: Calculate the voltage across R_L resistor in the network using Millmann's theorem?

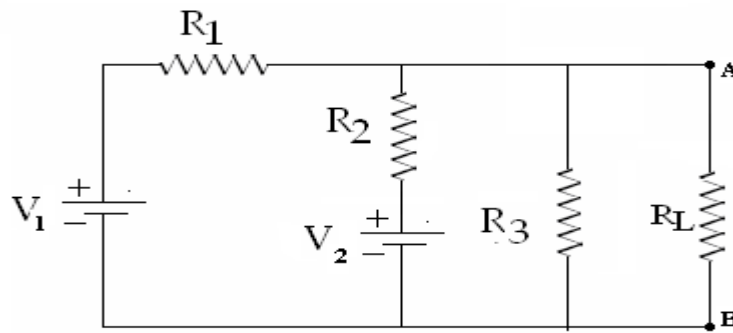

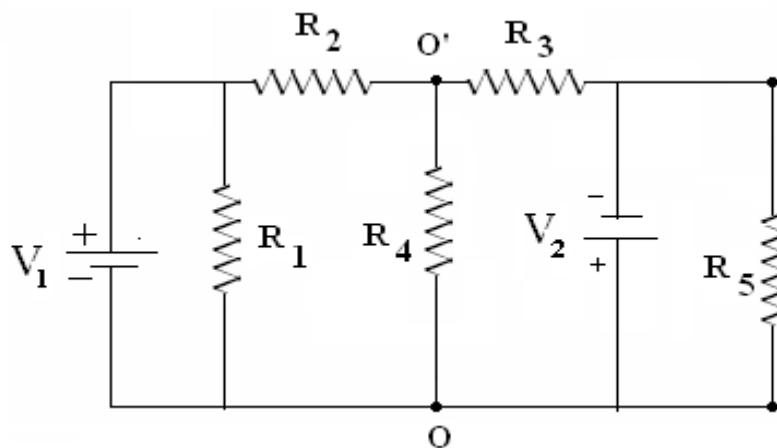
Question 2: use Millmann's theorem to calculate the voltage developed across the load resistor R_L in the network?




COMPENSATION THEOREM

Practice Problems

Question 1: If the resistance of R_2 branch increases to $(R_2 + \Delta R) \Omega$, determine the compensation source and verify the results?

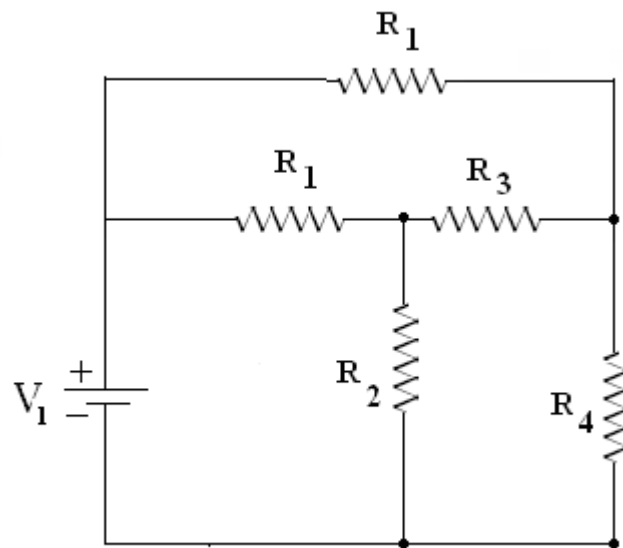

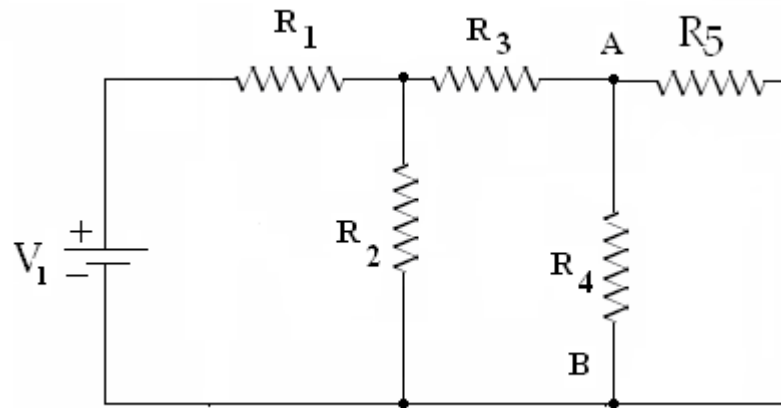
Question 2: verify the compensation theorem if there is a change in R_4 resistor due to the temperature variation ?



Admittance, Impedance , Transmission, and Hybrid Parameters

Practice Problems:

Question 1: Find out the Parameters for the below circuits?

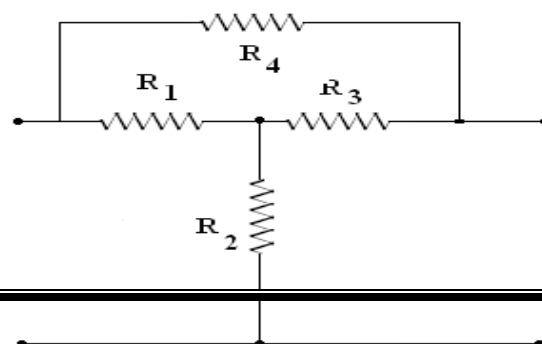

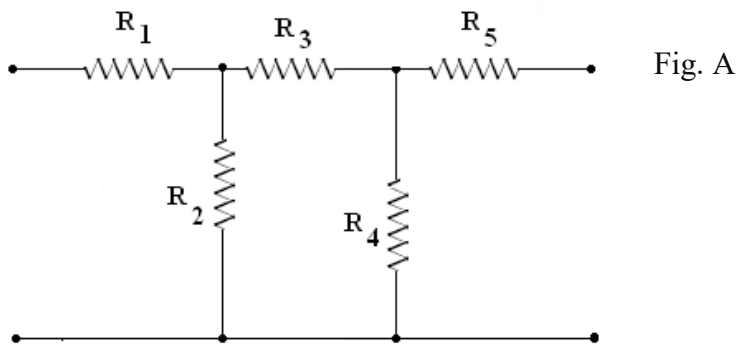


Fig. B

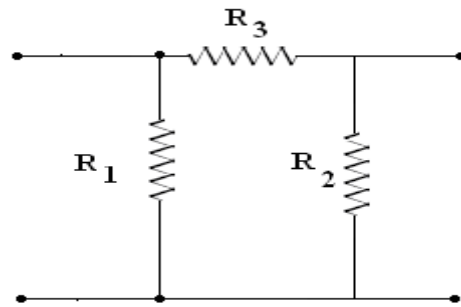


fig.C

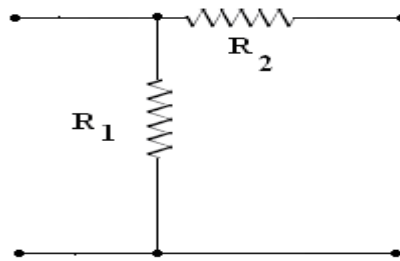


Fig. D

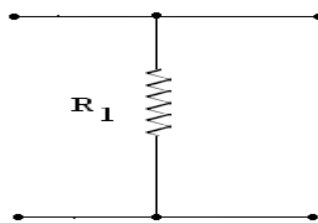


Fig. E

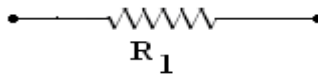


Fig. F

SELF AND MUTUAL INDUCTANCE OF A COUPLED COIL

Aim: To Determine the self and mutual inductance of a given coupled coil and also to determine the coefficient of coupling(K)

Apparatus Required:

Sl.no	Name of the equipment	Range/Type	Quantity
1	Single phase Supply	(0-230V)/5A,	

		50Hz	
2	Voltmeter	(0-300)V / MI	1 no.
3	Ammeter	(0-5) A /MI	1 no.
4	Wattmeter	300V, 5A, LPF	1 no.
5	1- Φ Transformer	230/115, 2KVA	1 no.
6	1- Φ Variac	(0-250)V / 6A	1 no.

Theory:

Circuit diagram to find Coefficient of coupling

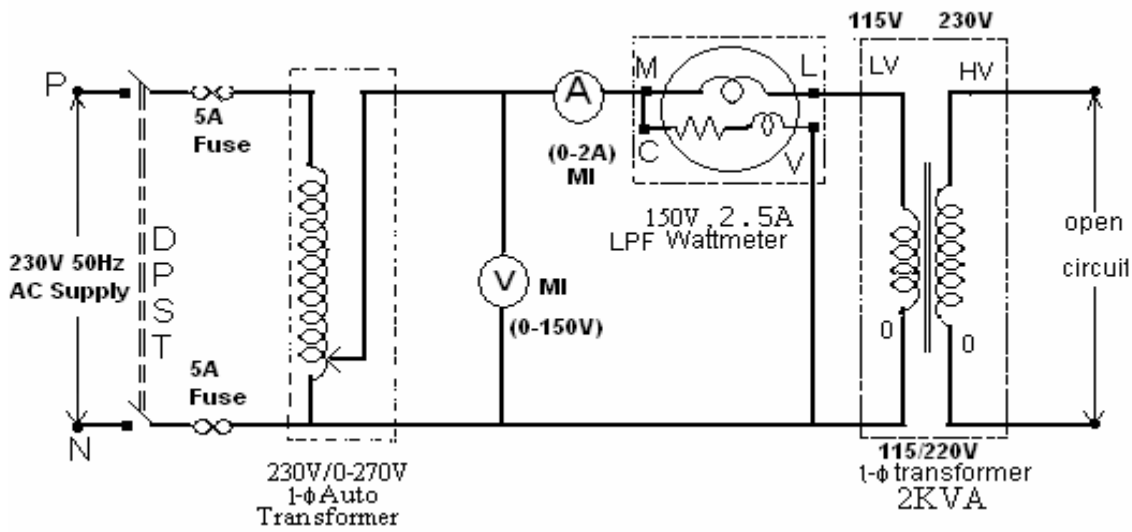


Fig. A

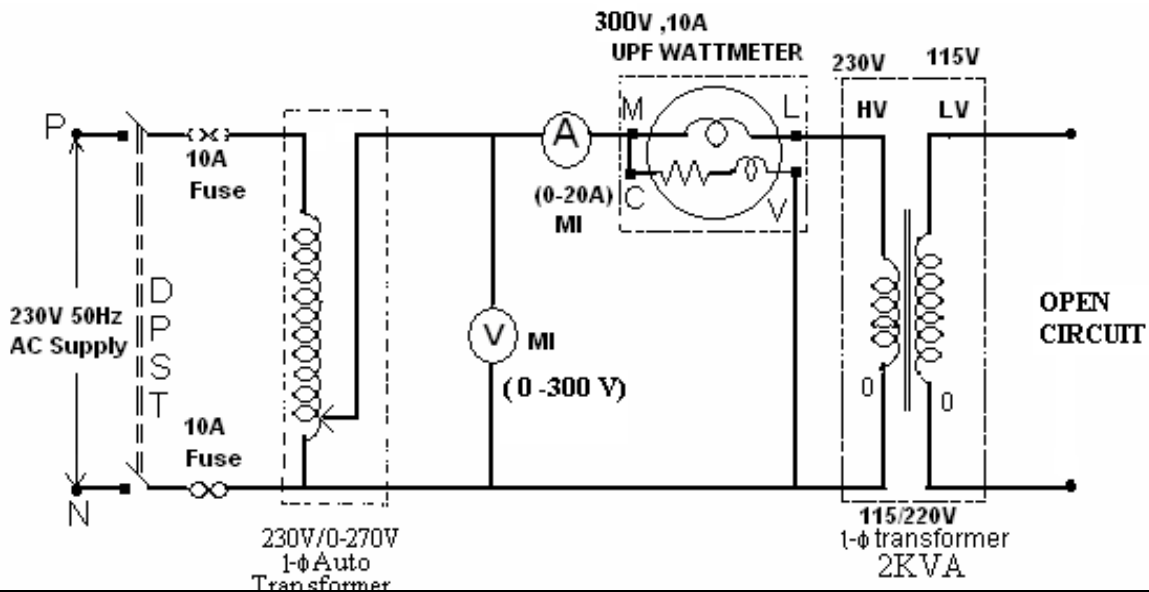


Fig.B

Procedure:

1. Make the connections as per the circuit diagram.
2. Apply different voltages to every winding with the help of 1- Φ variac. Note down the reading of ammeter, Voltmeter and wattmeter.
3. Calculate Coreloss current (I_c)

$$I_c = I_o \cos \Phi_o$$

$$W_o = V_1 I_o \cos \Phi_o$$

$$\cos \Phi_o = W / (V_1 * I_o)$$

$$\text{Magnetising Current } (I_m) = \sqrt{(I_o^2 - I_c^2)}$$

$$E_1 = j\omega M I_m$$

$$M = E_1 / (j\omega I_m) = E_1 / (2\pi f I_m)$$

3. Calculate inductance on load side

$$L_{LV} = V_1 / (2 * \pi * f * I_m)$$

4. Make the connections as shown in the figure(b). apply Different Voltages to the HV windings, and note down thw readings of ammeter, Voltmeter and wattmeter in a tabular column.
5. Calculate the magnetizing current (I_m) by applying tha above formula.
6. Caqlculte the inductance (L) and mutual inductance (M) on the LV side.

$$L_{HV} = V_2 / (2\pi f I_m)$$

$$M = E_1 / (2\pi f I_m)$$

$$L_{HV} = V_2 / (2\pi f I_m)$$

$$M = E_2 / (2\pi f I_m)$$

7. Calculate the coefficient of coupling (K)

$$K = M / \sqrt{(L_{HV} L_{LV})}$$

Theoretical Formulae:

For Figure (a):

$$I_c = I_o \cos \Phi_o$$

$$W_o = V_1 I_o \cos \Phi_o$$

$$I_m = \sqrt{I_o^2 - I_c^2}$$

$$M = E_1 / (2\pi f I_m)$$

$$L_{LV} = V_1 / (2 * \pi * f * I_m)$$

For Figure(b):

$$I_c = I_o \cos \Phi_o$$

$$W_o = V_1 I_o \cos \Phi_o$$

$$I_m = \sqrt{I_o^2 - I_c^2}$$

$$M = E_2 / (2\pi f I_m)$$

$$L_{HV} = V_1 / (2 * \pi * f * I_m)$$

Table 1:

s.no	V ₁ (V)	E ₁ (V)	I _o (A)	W _o (W)	I _c (A)	I _m (A)	M(H)	L _{LV} (H)

Table 2:

s.no	V ₂ (V)	E ₂ (V)	I _o (A)	W _o (W)	I _c (A)	I _m (A)	M(H)	L _{HV} (H)

Result:

The self and Mutual Inductance of a given coupled coil are calculated and the co-efficient of coupling (K) is also calculated.

SERIES AND PARALELL RESONANCE

Series Resonance


Aim: To obtain the resonance frequency, frequency curve, bandwidth, quality factor.

Apparatus Required:

Sl.no	Name of the equipment	Range/Type	Quantity
1	Function Generator & CRO Probes	-----	1 no
2	Digital Multimeter	-----	1 no.
3	Resister	1 K ohm	1 no.
4	Inductor	100 mH	1 no.
5	Capacitor	5uF	1 no.
6	Connecting wires	-----	

			Required
--	--	--	----------

Circuit Diagram:

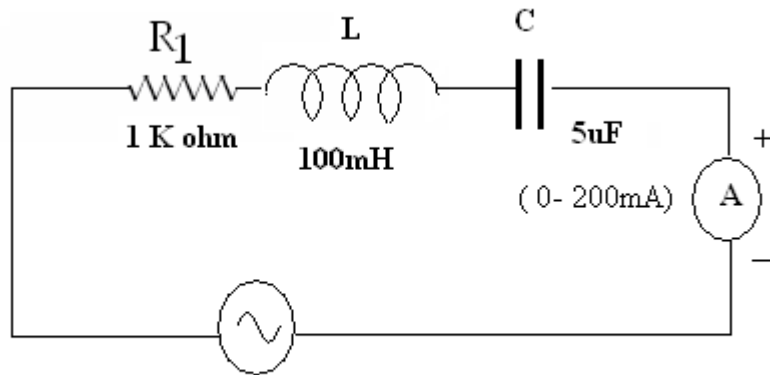

5V P-P F=1 KHZ


Procedure:

1. R, L, & C are connected in series with selected values of RLC as shown in figure.
2. Calculate the resonant frequency using the formula at selected values of L & C
3. Vary the frequency (below & above the resonant frequency)
4. Note down the corresponding readings of ammeter.
5. Now draw the frequency response characteristic curve taking the reading of frequency and current into consideration.

Theoretical Calculation:

- * $f_r = \frac{1}{2\pi\sqrt{LC}}$
- * $Q = \frac{\omega_r L}{R}$
- * $\omega_r = 2\pi f_r$
- * Band Width = f_r / Q

Model Graph:

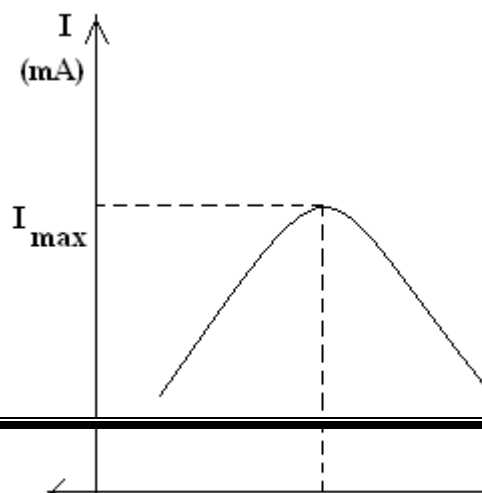

Tabular Column

Sl. No	Frequency (Hz)	I (mA)


Result: For the given series RLC circuit bandwidth, quality factor are calculated theoretically and practically and frequency response characteristics are obtained.

Parallel Resonance

Aim: To obtain the resonance frequency, frequency curve, bandwidth, quality factor.

Apparatus Required:

Sl.no	Name of the equipment	Range/Type	Quantity
1	Function Generator & CRO Probes	-----	1 no
2	Digital Multimeter	-----	1 no.
3	Resister	1 K ohm	1 no.
4	Inductor	100 mH	1 no.
5	Capacitor	5uF	1 no.
6	Connecting wires	-----	Required

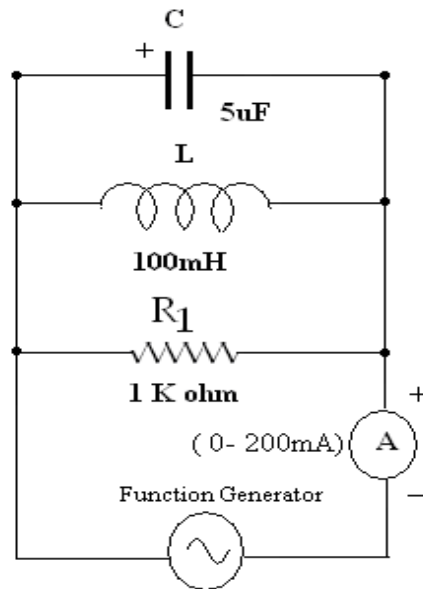Circuit Diagram:


5V P-P F=1 KHZ

Procedure:

1. R, L, & C are connected in parallel with selected values of RLC as shown in figure.
2. Calculate the resonant frequency using the formula at selected values of L & C
3. Vary the frequency (below & above the resonant frequency)
4. Note down the corresponding readings of ammeter.
5. Now draw the frequency response characteristic curve taking the reading of frequency and current into consideration.

Theoretical Calculation:

- * $f_r = \frac{1}{2\pi\sqrt{LC}}$
- * $Q = \frac{\omega_r L}{R}$
- * $\omega_r = 2\pi f_r$
- * Band Width = f_r / Q

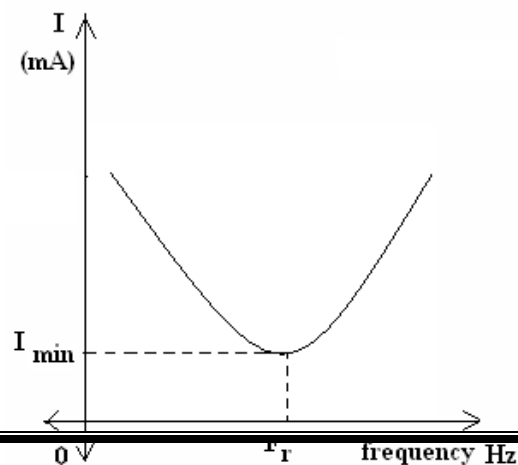Model Graph:

abular Column

Sl. No	Frequency (Hz)	I (mA)

Result: For the given parallel RLC circuit bandwidth, quality factor are calculated theoretically and practically and frequency response characteristics are obtained.

**TITLE: MEASUREMENT OF ACTIVE POWER CONSUMED BY 3- Φ
BALANCED STAR AND DELTA LOAD**

Aim: To measure active power and power in a balanced 3- Φ circuit using two single phase wattmeter's.

Apparatus required:

Sl.No	Name of the Equipment	Range	Type	quantity
1	3- Φ power supply 415 v , 50 Hz			--
2	3- Φ Auto transformer 415v , 50Hz	0-460v		1 No
3	ammeter	0-20 A	MI	1 No
4	voltmeter	0-600v	MI	1 No
5	Wattmeter	0-10A,	UPF,MI	2 No.
6	3- Φ variable load	----	-----	1 No.
7	Connecting wires			Required

Theory:

Total power consumed by 3- Φ balanced load can be measured by using two watmeters.

The wattmeter's consists of two coils namely pressure coil(PC) and current coil(CC).

The current coils are connected with any two of the lines say R and B. the pressure coils of the two wattmeters are connected between that line and the second line.i.e. Y line.

Considering a balanced 3- Φ load at a PF $\cos\Phi$ lagging, the three line currents I_R , I_Y & I_B will have the same magnitude and each will be lagging by angle Φ its corresponding voltage.

Assuming a Y connected system we have $I_L=I_{ph}$ and $V_L=\sqrt{3} V_{ph}$. Thus we have $I_R=I_Y=I_B=I_{ph}$. Similarly, for the voltages, $V_R = V_Y = V_B = V_{ph}$.

We know that the line voltages $V_{RY}= V_R-V_Y$, and line Voltage $V_{BY}=V_B-V_Y$. By phasor method we can determine line voltage V_{RY} V_{BY} as shown in fig. The line V_{RY} is seen to be leading V_R by 30° and line voltage V_{BY} seen to be lagging V_B by 30° . Thus the phase angle between the line voltage V_{RY} and line current I_R is $30^\circ + \Phi$. Similarly, the phase angle between the line voltage V_{BY} and line current I_B is $30^\circ+\Phi$. Therefore, the power in 2 wattmeters is given by,

$$W_1=V_{RY}*I_R*\cos (30^\circ + \Phi) = \sqrt{3} V_{ph} I_{ph} \cos (30^\circ + \Phi).$$

$$W_2=V_{BY}*I_B*\cos (30^\circ - \Phi) = \sqrt{3} V_{ph} I_{ph} \cos (30^\circ - \Phi).$$

The addition of two powers gives

$$W_1 + W_2 = \sqrt{3} V_{ph} I_{ph} \cos (30^\circ + \Phi) + \sqrt{3} V_{ph} I_{ph} \cos (30^\circ - \Phi).$$

$$= 3 V_{ph} I_{ph} \cos \Phi.$$

For 'Y' load:

$$V_{ph} = V_L / \sqrt{3}, I_{ph} = I_L$$

$$W_1 + W_2 = 3 (V_L / \sqrt{3}) I_L \cos \Phi = \sqrt{3} V_L I_L \cos \Phi$$

For 'Δ' load:

$$V_{ph} = V_L, I_{ph} = I_L / \sqrt{3}$$

$$W_1 + W_2 = 3 V_L (I_L / \sqrt{3}) \cos \Phi = \sqrt{3} V_L I_L \cos \Phi$$

Power factor

$$W_1 = \cos (30^\circ + \Phi)$$

$$W_2 = \cos (30^\circ - \Phi)$$

$$W_1 - W_2 = \cos (30^\circ + \Phi) - \cos (30^\circ - \Phi)$$

$$W_1 + W_2 = \cos (30^\circ + \Phi) + \cos (30^\circ - \Phi)$$

$$= \frac{2 \sin 30^\circ \sin \Phi}{2 \cos 30^\circ \cos \Phi} = \tan 30^\circ \tan \Phi$$

$$\left[\quad \quad \right]$$

$$\left[\quad \quad \right]$$




$$\text{TAN } \Phi = \sqrt{3} \frac{W1 - W2}{W1 + W2}$$


$$\Phi = \text{TAN}^{-1} \sqrt{3} \left[\frac{W1 - W2}{W1 + W2} \right]$$

CIRCUIT DIAGRAMS

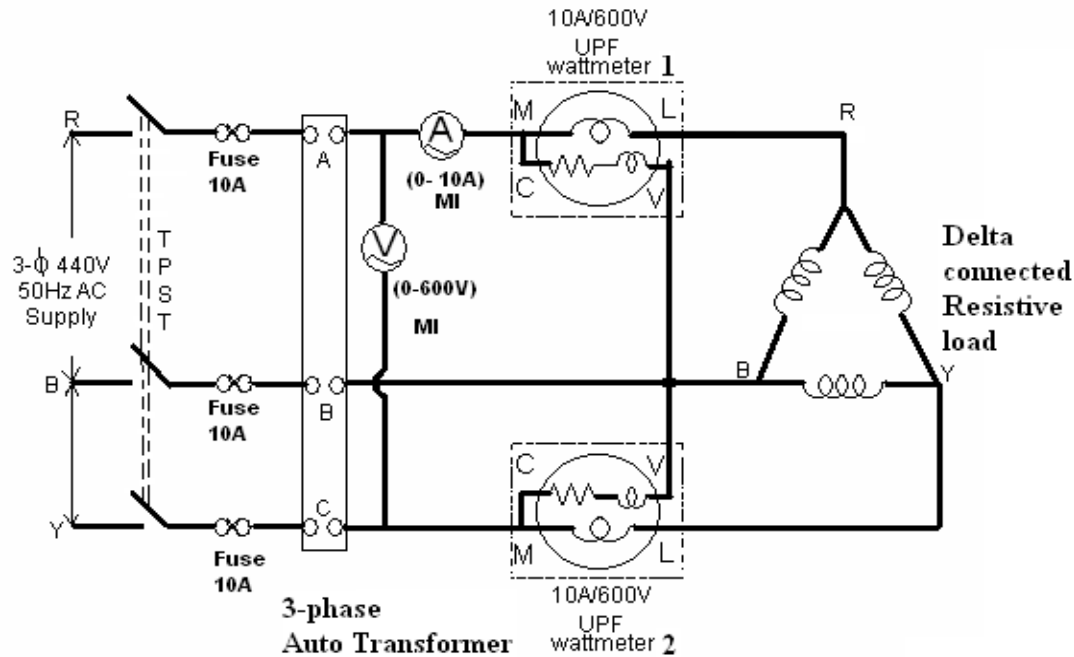Circuit diagram for Delta connected diagram



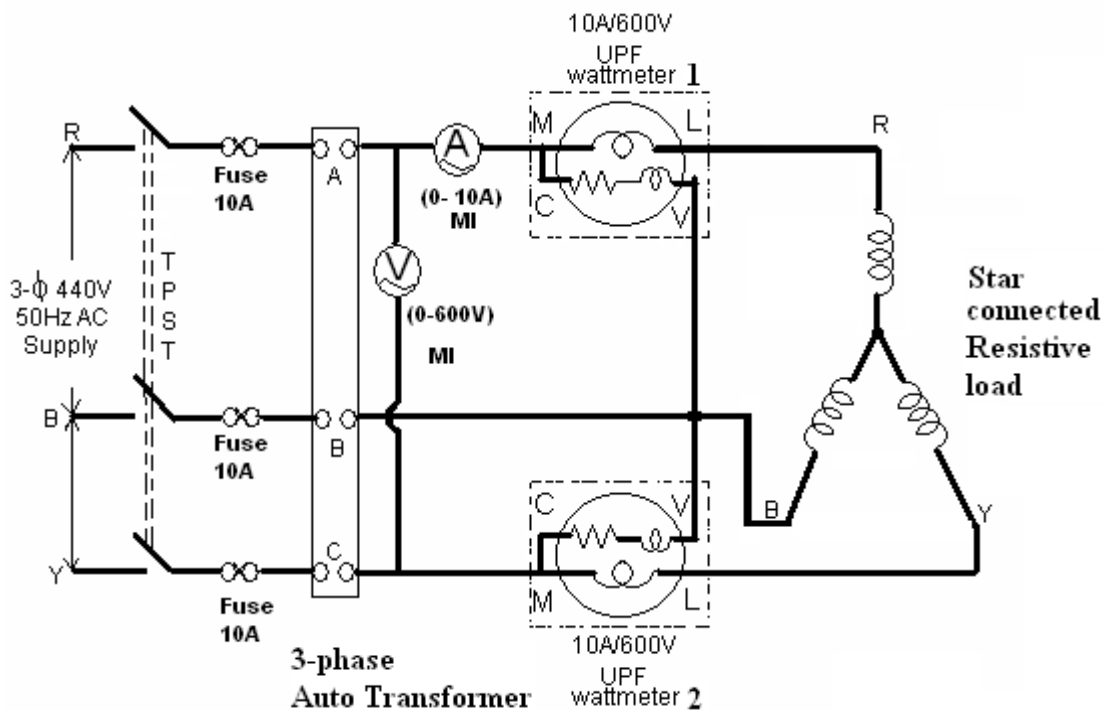Circuit diagram for Star connected diagram



PROCEDURE:

- 1) Make the connections as shown in figure.
- 2) Keep the three phase auto transformer at its zero position.
- 3) Keep the three phase variable load so as to have maximum impedance.
- 4) Switch ON the 3- Φ supply mains.
- 5) Increase the voltage supplied to the circuit by changing the position of variac so that all the meters give readable deflection.
- 6) Note down the readings of all meters.
- 7) Change the supply voltage and repeat the step 5 and 6 for at least 5 times.
- 8) If changing the supply voltage does not give sufficient number of readings the 3- Φ load can also be changed to take different readings.
- 9) Decrease the voltage supplied to the circuit autotransformer.
- 10) Switch OFF the supply.

Precautions:

1. All the connections should be tight.
2. The readings in ammeters should not exceed the current ratings of wattmeters.
3. During the experiment one of the wattmeters may give give negative deflection. In this case the connections of either the current coil or the pressure coil of the wattmeter should be reversed, the wattmeter will give positive deflection. The reading of that wattmeter should now be recorded with negative sign.

Observations:

Sl.no	V (volts)	I (amp)	W1 (watts)	W2 (watts)	$P = W1+W2$ (watts)	$P = W1-W2$ (watts)	$\text{COS } \Phi$ (deg)

Results:

EXPERIMENT**DETERMINATION OF SELF, MUTUAL INDUCTANCE AND COEFFICIENT OF COUPLING****AIM:**

To determine self, mutual inductance and coefficient of coupling of a mutually coupled circuit.

APPARATUS:

S. No.	Name of the Equipment	Range	Type	Quantity
1	Ammeter			
2	Voltmeter			
3	1-phase Transformer			
4	1-phase Variac			
5	1-ph A.C. Supply			
6	Connecting Wires			

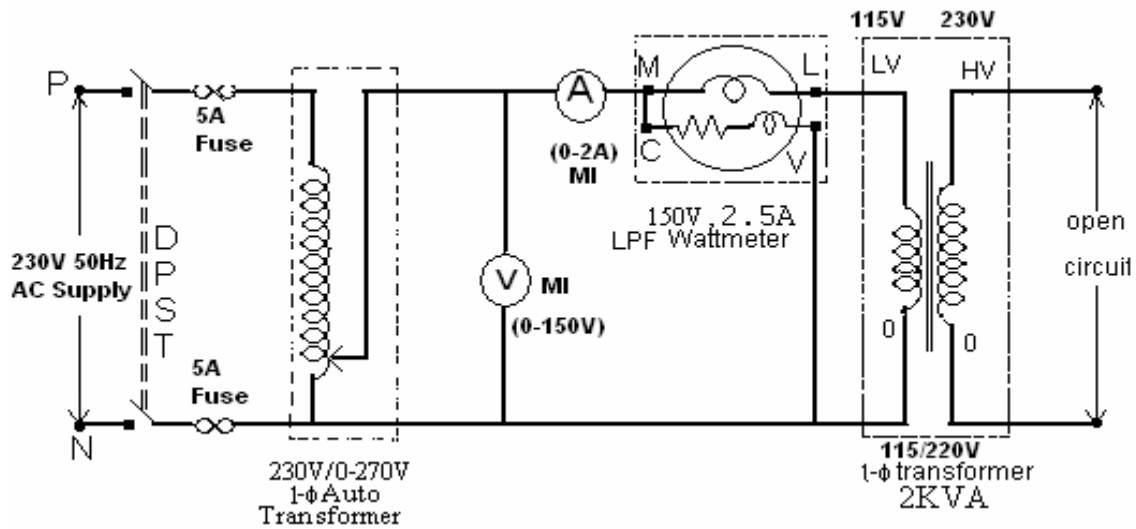
Circuit diagram:

Fig. A

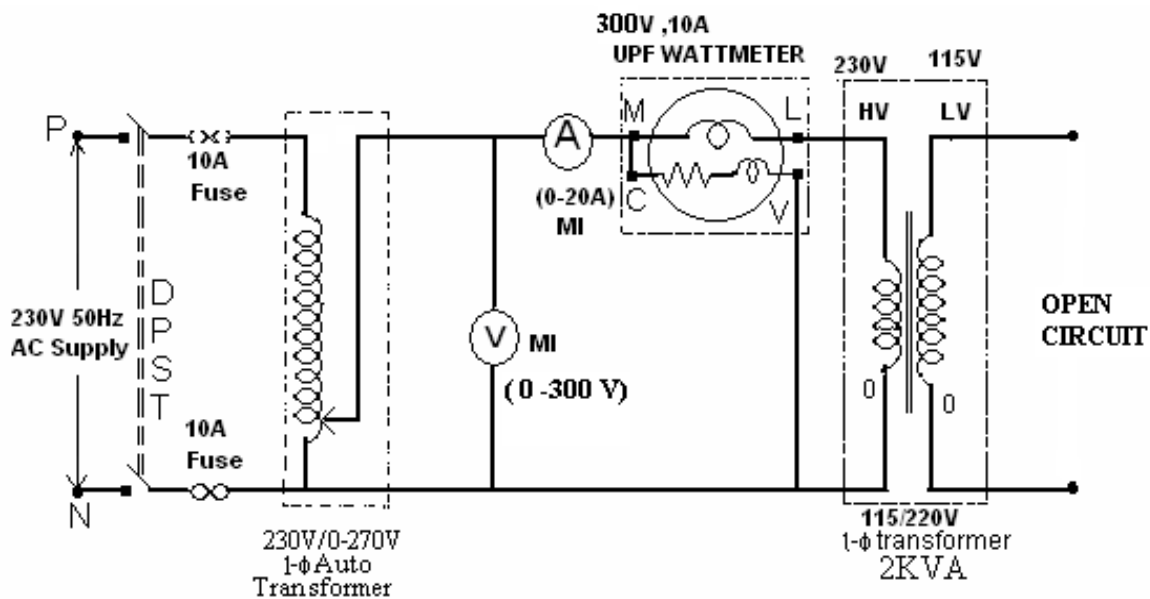


Fig.B

14.1 PROCEDURE:

1. Connect the circuit as shown in fig.14.1 and measure the self inductance of coil 1 i.e. L₁ by noting the voltmeter and ammeter readings.
2. Connect the circuit as shown in fig.14.2 and measure the self inductance of coil 2

i.e. L_2 by noting the voltmeter and ammeter readings.

3. Connect the circuit as shown fig.14.3 and note down voltmeter (V) and ammeter (A) readings and determine equivalent inductance L_{eq} .
4. Calculate coefficient of coupling.

14.2 THEORETICAL CALCULATIONS:

(Neglect winding resistance) $L_{eq} = L_1 + L_2 \pm 2M$

Mutual Inductance $M = [(L_{eq} - (L_1 + L_2))/2]$

Coefficient of Coupling $K = M/\sqrt{(L_1 L_2)}$ Where L_1 and L_2 are determined as follows

Determination of L_1

From fig.A

$X_{L1} =$ voltmeter reading

/ammeter reading $X_{L1} = \omega L_1$

$= 2\pi f L_1$

$L_1 = X_{L1}/2\pi f$ (Henry)

Determination of L_2

From fig B

$X_{L2} =$ Voltmeter reading /Ammeter reading $X_{L2} = \omega L_2 = 2\pi f L_2$

$L_2 = X_{L2}/2\pi f$ (Henry)

Determination of L_{eq}

From fig 14.3

$X_{Leq} =$ Voltmeter reading

/Ammeter reading $X_{Leq} =$

$\omega L_{eq} = 2\pi f L_{eq}$

$L_{eq} = X_{Leq}/2\pi f$ (Henry)

TABULAR COLUMN: For X_{L1}

S. No.	Voltmeter Reading	Ammeter Reading	$X_{L1} = V/I$
1			

2			
3			
4			

For XL2

S. No.	Voltmeter Reading	Ammeter Reading	$X_{L2} = V/I$
1			
2			
3			
4			

For Xeq

S. No	Voltmeter Reading	Ammeter Reading	$X_{Leq} = V/I$
1			
2			
3			
4			

RESULT:

PRE LAB VIVA QUESTIONS:

1. What is self inductance?
2. What is mutual inductance?
3. Define coefficient of coupling.
4. What is the formula for coefficient of coupling?
5. Define self induced emf.
6. Define mutually induced emf.

LAB ASSIGNMENT:

7. Derive the expression between self inductance of two coils, mutual inductance between them and coefficient of coupling.
8. State and explain Faraday's law of electromagnetic induction.
9. Two coils of self inductances L1 and L2 are connected in series and M is the

mutual inductance between them, derive the expression for the net inductance of the coil.

POST LAB VIVA QUESTIONS:

10. Using dot convention, discuss the coupling in a simple magnetic circuit?
11. What is statically induce emf and dynamically induce emf?
12. Compare electric and magnetic circuit.
13. What is Lenz's law?

PSPICE

INTRODUCTION

The acronym **PSPICE** stands for - *Simulation Program with Integrated Circuit Emphasis*.

SPICE is a general purpose circuit diagram that simulates electronics circuits. Spice can perform various analyses of electronics circuits namely operating point of transistor, a time domain response, a small signal frequency response etc. It is a versatile program.

It contains certain models for common circuit elements, active as well as passive and is capable of simulating most electronic circuits.

The algorithms of spice are general in nature but are robust and powerful for simulating electrical and electronics circuits. The input syntax for spice is a free format style, it does not require that data be entered in fixed columns locations. Spice assumes reasonable default values for unspecified circuit parameters. In addition, it performs considerable amount of error checking to ensure that a circuit has been entered correctly.

A circuit is described by statements that are stored in a file called *circuit file*. It is normally typed from the keyboard. The circuit file is read by Pspice simulator. Each statement is self contained and independent, the statements do not interact with each other.

The circuit file contains the circuit details of components and elements, the information about the sources and the command for what to calculate and what to provide as output.

The circuit file is the input file to the Spice program which after executing the commands, produces the results in another file called the *output file*.

Types of analysis : PSpice allows various types of analysis

DC Analysis: It is used for circuits with time –invariant sources. It calculates all node voltages and branch currents over a range of values.

.DC --- DC sweep of an input voltage / current source over a range of values

.OP --- DC operating point to obtain all node voltages

Transient analysis: It is used for circuits with time variant sources. It calculates all node voltages and branch currents over a time interval, and their instantaneous values are the outputs.

.TRAN --- circuit behaviour in response to time varying sources.

AC analysis: It is used for small signal analysis of circuits with sources of variable frequencies. It calculates all node voltages and branch currents over a range of frequencies.

.AC --- circuit over arrange of source frequencies.

Circuit description:

A circuit must be specified in terms of elements names, element values, nodes, variable parameters and sources.

For a circuit that is to be simulated for calculating all node voltages and currents, the user has to show the required:

- 1) How to describe this circuit to spice.
- 2) How to specify the type of analysis to be performed
- 3) How to define the required output variables.

Element values:

The element values are written in standard floating point notation with optional scale and unit suffixes. There are two types of suffixes: scale suffix , unit suffix.

RECOGNISED SCALE SUFFIXES:

N=1E-9, U =1E-6, M=1E-3, K=1E3, 1MEG=1E6,

RECOGNISED SCALE SUFFIXES:

V=volt, A=amp, HZ=hertz, OHM=ohm, H= henry, F= farad, DEG=degree

NODES:

The location of the element is identified by the node numbers. Each element is connected between two nodes. Node numbers are assigned in the circuit. Node 0 is predefined as ground.

The node numbers to which an element is connected are specified after the name of an element.

Format for describing passive elements:

< element name > < positive node > < negative node > < value >

Symbols of circuit elements and sources;

C-----capacitor

D-----Diode

I-----Independent current source

L-----Inductor

R-----Resistor

V-----Independent Voltage source

Format for describing source elements :

< source name > < positive node > < negative node > < source model >

The model for a simple dc source is : DC < value>

Ex: VS 1 0 DC 20V

Output variables:

To print or plot output voltages or currents spice permits certain types.

V(4,0) – voltage of node 4 w.r.t to node 0 i.e, ground.

Spice can give the current of a voltage source as an output by dummy voltage source of 0V

VX 3 0 DC 0V ; measures current through node 3 element.

Commands:

.PROBE : Probe is a *graphical waveform analyzer* for PSpice

.PLOT : This command generates the plot on the output file

.PRINT : This command gives a table of data on the output file

.END : End of file statement


TITLE: SIMULATION OF DC CIRCUIT

Aim: To simulate the circuit on Pspice and to find out the node voltages and respective branch currents.

Software: PSPICE

Version: MICROSIM EVALUATION 8.0

Circuit diagram:

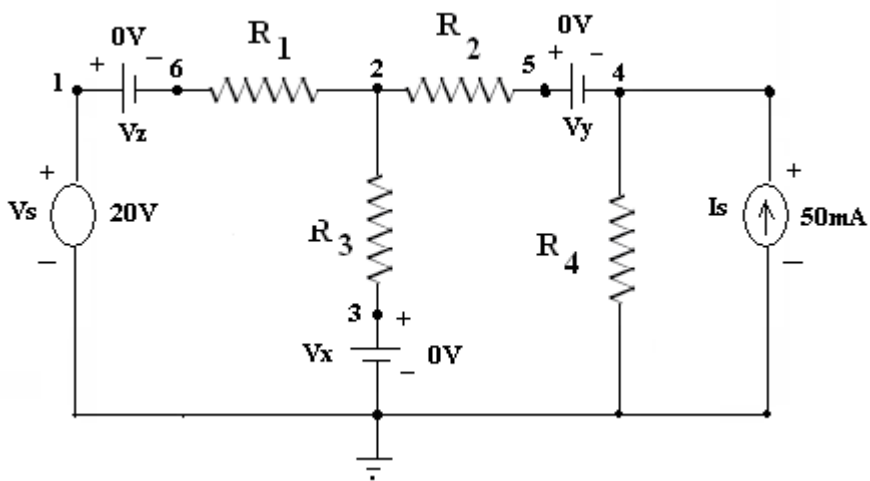

Program:

VS 1 0 DC 20V

IS 0 4 DC 50MA

R1 6 2 500

R2 2 5 800

R3 2 3 1KOHM

R4 4 0 200

VX 3 0 DC 0V


```
VY 5 4 DC 0V
VZ 1 6 DC 0V
.DC VS 10V 30V 10V
.PRINT DC V(4) I(VX) I(VY) I(VZ)
.END
```

Output file

RESULT:

THEORITICAL CALCULATIONS:

Note :File name is given with < *file name .cir* >extension


TITLE : TRANSIENT RESPONSE OF A DC CIRCUIT

Aim: To find the dc transient response of a series RLC circuit for a PULSE input.

Software: PSPICE

Version: MICROSIM EVALUATION 8.0

Circuit diagram:

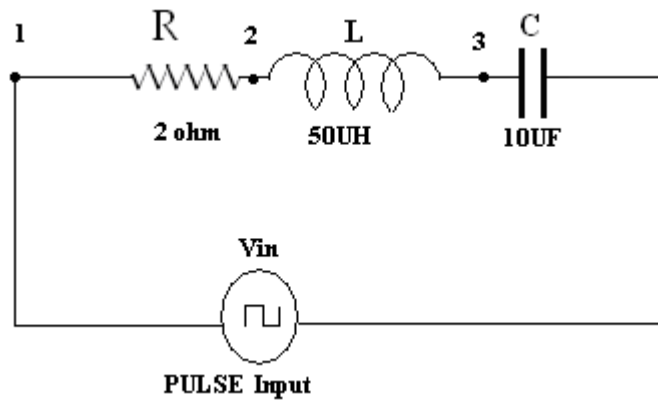

Program:

```
VIN 1 0 PULSE(-220 220 0 0 1NS 1NS 100US 200US)
```

```
R1 1 2 2
```

```
L1 2 3 50UH
```

```
C1 3 0 10UF
```

```
.TRAN 1US 400US
```

```
.PROBE
```

```
.END
```

Output file:

RESULT:


DC TRANSIENT RESPONSE OF A SERIES RLC CIRCUIT FOR A STEP INPUT.

Aim: To find the dc transient response of a series RLC circuit for a STEP input.

Software: PSPICE

Version: MICROSIM EVALUATION 8.0

Circuit diagram:

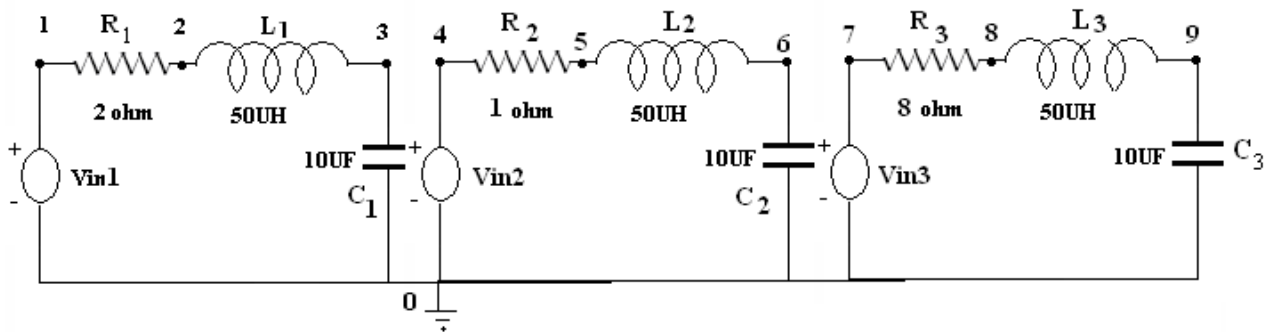

Program:

```

VII 1 0 PWL (0 0 1NS 1V 1MS 1V)
VI2 4 0 PWL (0 0 1NS 1V 1MS 1V)
VI3 7 0 PWL (0 0 1NS 1V 1MS 1V)
R1 1 2 2
L1 2 3 50UH
C1 3 0 10UF
R2 4 5 1
L2 5 6 50UH
C2 6 0 10UF
R3 7 8 8
L3 8 9 50UH
C3 9 0 10UF
.TRAN 1US 400US
.PROBE
.END

```

Output file:

RESULT:


DC TRANSIENT RESPONSE OF A SERIES RLC CIRCUIT FOR A SINE INPUT

Aim: To find the dc transient response of a series RLC circuit for a SINE input.

Software: PSPICE

Version: MICROSIM EVALUATION 8.0

Circuit diagram:

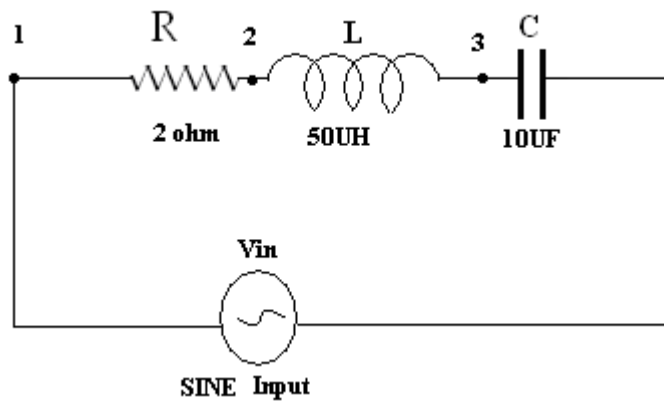**Program:**

```
VIN 1 2 SIN(0 10V 5KHZ)
R1 1 2 2
L1 2 3 50UH
C1 3 0 10UF
.TRAN 1US 500US
.PLOT TRAN V(3) V(7)
.PROBE
.END
```

Output file:**RESULT:**

Harmonic Analysis and Determination of Form Factor

AIM:-


Sl.No	Experiment Name
1	Harmonic Analysis of non-sinusoidal waveform signals using Harmonic Analyzer and plotting spectrum.
2	Determination of form factor for non-sinusoidal waveform

APPARATUS REQUIRED:-

Si.No	Apparatus name	Qty
01	Harmonic Analyzer (THDPM-1)	01
02	Test bench setup	01
03	LED bulb 5W	01
04	CFL Bulb 15W	01
05	Connecting wires.	As required

THEORY:-

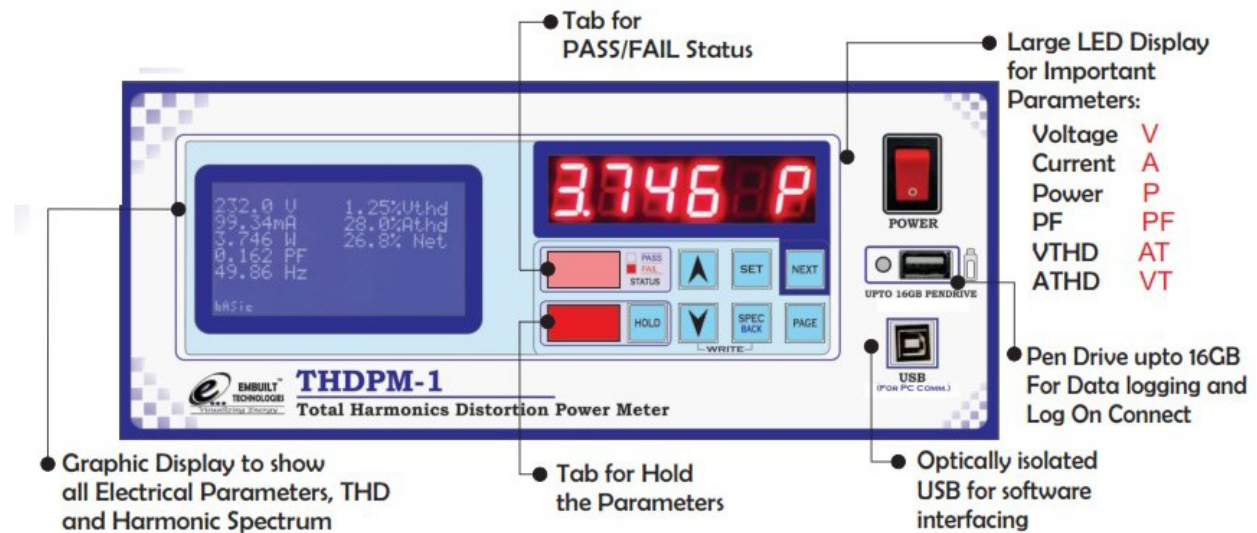By using Total Harmonics Distortion Power Meter we can analyze the harmonics present in different types of electrical apparatus.



Harmonics can be analyzed for both Voltage and Current Waveforms. Up to 55th Harmonics can be seen on the THDPM-1 in tabulated and Bar Graph Form.



There are two types of Harmonics analysis done:

1. Testing the Harmonics of Incoming Voltage.
eg. Comparing the Harmonics of Square Wave Inverter and Sine Wave inverter
2. Testing the Harmonics of different loads. This is done in ideal conditions.
In non-Industrial environment, the Electricity Board harmonics are normally low and can be used for this type of experiments.

eg. Harmonics of a Bulb, Harmonics of a LED Bulb.

Technical Description:

Auxiliary Supply : 180 – 240 Volts

Input Voltage : 3V – 300 Volts

Current : 10mA – 2 Amps

Frequency 45-55 Hz

Measures up to 55th Harmonic

Accuracy Class: 0.2%

Voltage Harmonics

Current Harmonics

- THDPM-1 is THD analyzer which measures up to 55th harmonic.

- It provides Voltage and Current THD.
- It shows the net effect on THD due to load.
- It also shows following parameters
 - Voltage
 - Current
 - Watt
 - Frequency
 - Power Factor
- It is useful for testing of LED Drivers, SMPS, CFL, CHOKES, Charger, AC to DC Converter, UPS etc.



Fig 1: Panel View

TEST BENCH SETUP

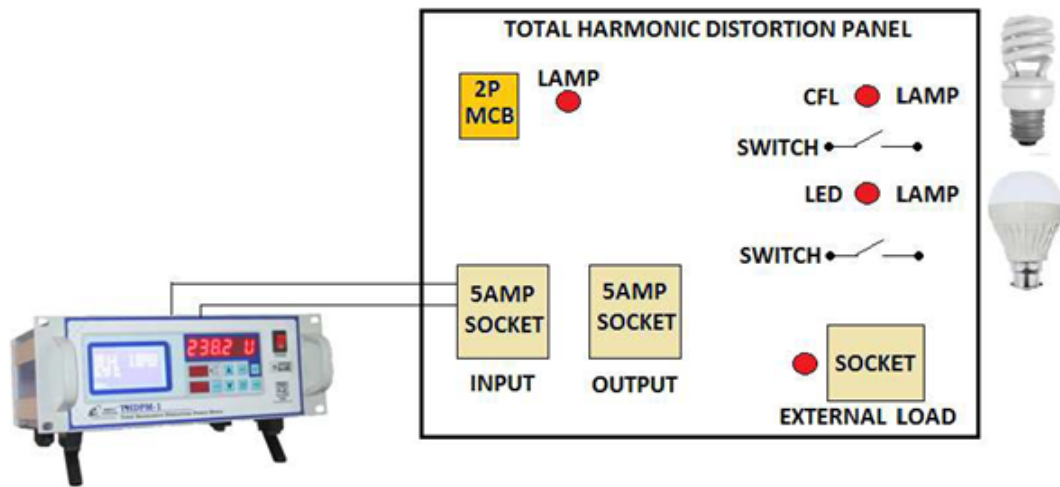


Fig 2: Test bench setup

Connection Diagram of THDPM-1 For Alternating Current Testing



Fig 3: Circuit Diagram

PROCEDURE:-For Experiment No: 1

HARMONIC ANALYSIS OF NON-SINUSOIDAL WAVEFORM SIGNALS USING HARMONIC ANALYZER AND PLOTTING SPECTRUM.

1. Switch ON the Harmonic Analyzerkit.
2. Connect the Circuit as per the circuit diagram as shown in fig.
3. Connect the source terminals of Harmonic Analyzer to source terminals provided on the panel.
4. Connect the Load terminals of Harmonic Analyzer to Load terminals provided on the panel.
5. Now, switch ON CFL bulb using switch provided.
6. Observe the readings displayed on Harmonic Analyzer kit main page.
7. Note down the voltage Harmonics and V_{THD} % level.
8. Note down the Current Harmonics and A_{THD} % level.
9. Tabulate the readings in tabular column.
10. Observe the Harmonic Spectrum graph displayed on Harmonic Analyzer kit.
11. Repeat the above procedure for LED bulb also.
12. Repeat the above procedure for CFL and LED bulb combination.

For Experiment No: 2

DETERMINATION OF FORM FACTOR FOR NON-SINUSOIDAL WAVEFORM

1. Switch ON the Harmonic Analyzerkit.
2. Connect the Circuit as per the circuit diagram as shown in fig.
3. Connect the source terminals of Harmonic Analyzer to source terminals provided on the panel.
4. Connect the Load terminals of Harmonic Analyzer to Load terminals provided on the panel.
5. Now, switch ON CFL/LED bulb using switch provided.
6. Observe the Form factor and crest factor displayed on Harmonic Analyzer.
7. Using the formula determine the form factor and note down the readings.

FOR DETERMINATION OF FORM FACTOR:

Peak Value (V_{pk}) = Reading taken from THD meter.

RMS Value (V_{rms}) = $V_{pk} \times 0.707$

Average Value (V_{avg}) = $V_{pk} \times 0.637$

$$\text{Crest Factor} = \text{Peak} / \text{RMS} = \frac{V_{pk}}{V_{pk} \times 0.707} = 1.414$$


$$\text{Form Factor} = \text{RMS} / \text{Avg} = \frac{V_{pk} \times 0.637}{V_{pk} \times 0.707} = 1.1098$$

**MAIN PAGE**

- Voltage, Current, Wattage, PF, Frequency
- Voltage THD, Current THD
- Net Effect of load on THD
- Model number
- Pass/Fail status





GRAPHICAL HARMONIC SPECTRUM VIEW

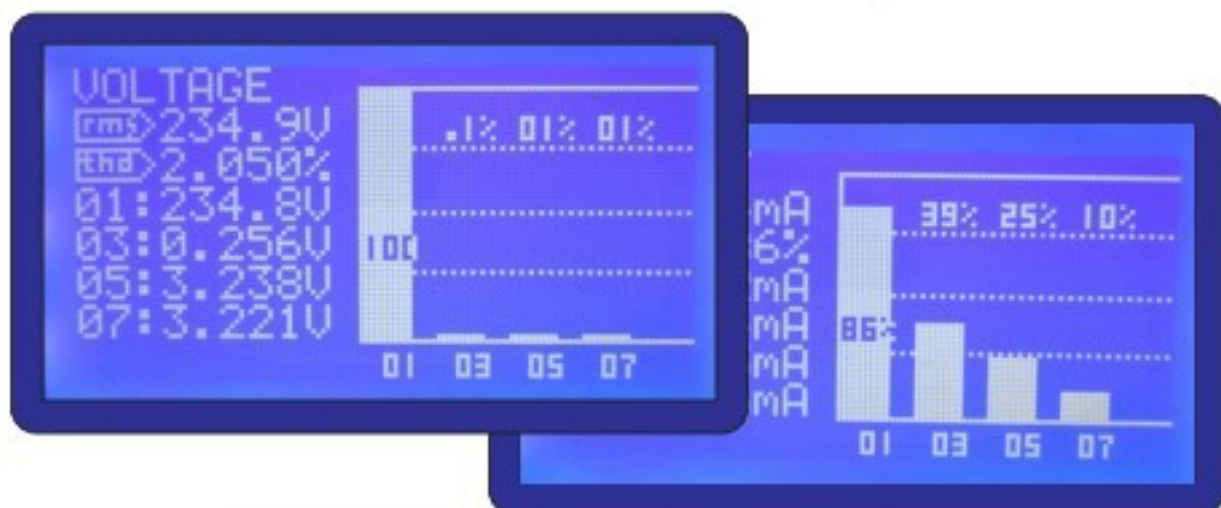

VOLTAGE & CURRENT THD PAGE

- RMS Value
- Total Harmonic Distortion
- Upto 55th order of Voltage/Current Harmonics

READINGS FROM THE THD METER:

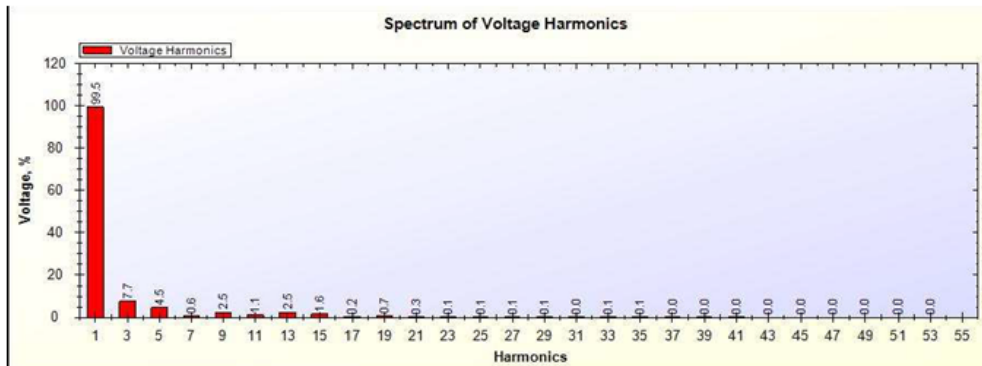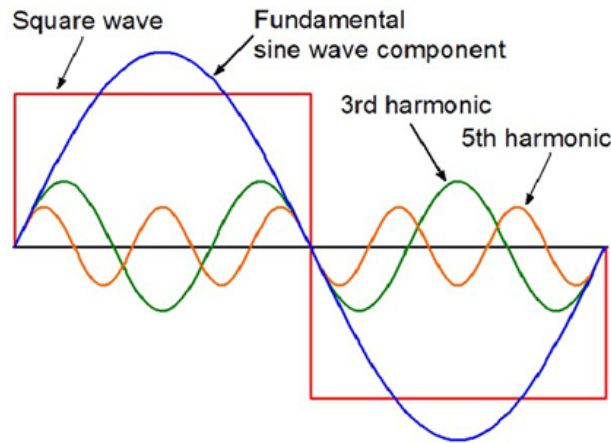

Voltage
 3rd Harmonic
 5th Harmonic
 7th Harmonic



Voltage rms Value
 1st Harmonic
 THD %

Voltage and Current Harmonics up to 55th Harmonics

OBSERVATION TABLES:-

Voltage:	
Current:	
Power:	
Power Factor:	
Frequency:	
V_{THD} %:	
A_{THD} %:	

Exp. 1

Type of load: LED bulb. (Voltage and Current Harmonics up to 55th Harmonics)

Harmonics	Voltage THD	Voltage THD %

Harmonics	Current THD	Current THD %

Exp. 2

Type of load: CFL bulb. (Voltage and Current Harmonics up to 55th Harmonics)

Harmonics	Voltage THD	Voltage THD %

Harmonics	Current THD	Current THD %

Exp. 3

Type of load: CFL & LED bulb. (Voltage and Current Harmonics up to 55th Harmonics)

Harmonics	Voltage THD	Voltage THD %

Harmonics	Current THD	Current THD %

For Experiment No: 2

□ DETERMINATION OF FORM FACTOR FOR NON-SINUSOIDAL WAVEFORM

**FOR DETERMINATION OF FORM FACTOR:**

Peak Value (V_{pk}) = Reading taken from THD meter.

RMS Value (V_{rms}) = $V_{pk} \times 0.707$

Average Value (V_{avg}) = $V_{pk} \times 0.637$

$$\text{Crest Factor} = \text{Peak} / \text{RMS} = \frac{V_{pk}}{V_{pk} \times 0.707} = 1.414$$

$$\text{Form Factor} = \text{RMS} / \text{Avg} = \frac{V_{pk} \times 0.707}{V_{pk} \times 0.637} = 1.1098$$